

Solve [Problem 1 or Problem 2 or Problem 3] and [Problem 4 or Problem 5 or Problem 6]

[2.5p]

[7.5p]

**Problem 1.**

- a) Analyse the circuit in Fig. 1 using a timing diagram, naming all the signals of interest and indicating sampled values.
- b) Find the binary codes (numbers) generated at the output vector Q(2..0).
- c) Discuss what will be the circuit's CLK maximum frequency of operation if flip-flop components are implemented internally as standard FSM. Typical CLK to output propagation time ( $t_{co}$ ) of a D\_FF is 3.7 ns. Typical propagation delay ( $t_p$ ) of a generic logic gate is 3.9 ns.

 


Fig. 1. Circuit based on flip-flops.

**Problem 2.**

Solve the combinational circuit presented in Fig. 2 using a PIC18F4520 microcontroller.

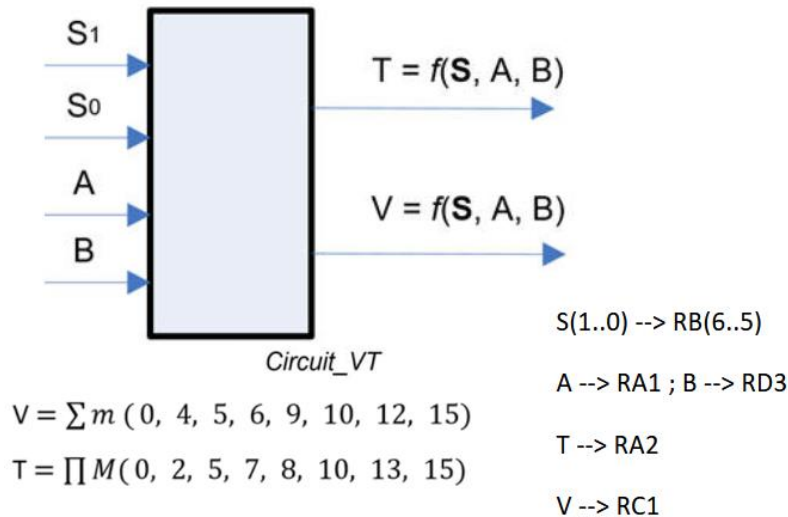


Fig. 2. Combinational circuit.

- a) Draw the hardware schematic including microcontroller reset and oscillator circuits.
- b) Organise the main program in our CSD way. Propose a hardware-software diagram naming all the electrical signals, RAM variables and software functions. Explain how to configure the  $\mu C$  in *init\_system()*.
- c) Organise and explain using a flowchart the interface function *read\_inputs()* and its bitwise operations.
- d) Organise using a flowchart the interface function *write\_outputs()* and its bitwise operations.
- e) Infer the *truth\_table()* software function using a behavioural interpretation and the corresponding flowchart.

**Problem 3.**

Invent a synchronous BCD down counter module 72 (*Counter\_BCD\_mod72*) with count enable (CE) and terminal count (TC72) using **plan C2** and standard components such *Counter\_mod16* (Fig. 3) and other circuits if necessary.

- a) Specifications: symbol, function table, timing diagram, state diagram.
- b) Planning schematics and components. How many *D\_FF* will include the *Counter\_BCD\_mod72* design?

 


Fig. 3. Symbol of the 4-bit standard universal binary radix-2 counter component (*Counter\_mod16*).

**Problem 4. LED lamp dimmer**

The luminaries that we use today work with high efficiency LED lamps and the light generated can be dimmed using a control circuit. Let us propose two alternative designs.

**Section 1. Hardware design (FPGA, VHDL).**

To modulate the light intensity we can use a simple pushbutton that produces a PWM waveform. In this example, let us fix five intensity levels as shown in Fig. 4. Every time that we click the up-button (UB) we generate a new intensity level from 0% (Lamp OFF) to 100% (Lamp ON, max light intensity).


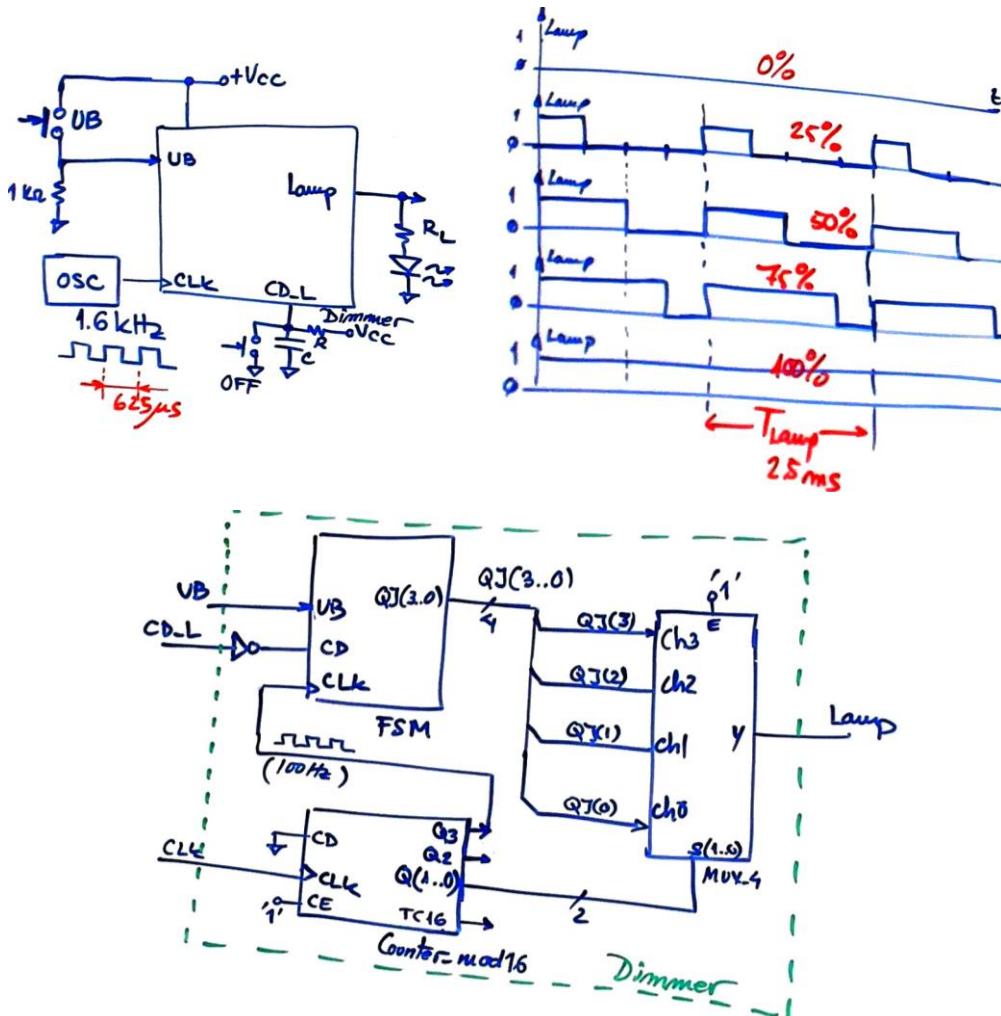


Fig. 4. Symbol, proposed internal schematic and waveforms generated for driving the Lamp.

- Explain how the proposed circuit in Fig. 4 works. Which Johnson codes are required to generate such PWM waveforms?
- Propose the FSM state diagram.
- Draw the FSM structure. Draw the state register schematic using  $D\_FF$ . Code the internal states in binary Gray. How many VHDL files are required to solve this plan C2 project?
- Propose the CC1 and CC2 truth tables and their flowcharts.
- Design a  $CLK\_Generator$  circuit to obtain the 1.6 kHz CLK from a 26 MHz crystal oscillator. How many  $D\_FF$  will contain the full *Dimmer* design?

**Section 2. Microcontroller design.**

- Draw a schematic to implement the *Dimmer* using a PIC18F4520 microcontroller. Draw the power-on reset (MCLR\_L) circuit and explain how it works. Draw the oscillator circuit using a 12 MHz quartz crystal.
- Adapt the state diagram so that it can be driven by interrupt flags.
- Draw the hardware-software diagram indicating the required RAM variables and how the FSM and shift operations (datapath) are solved in software. Organise the main program as a FSM in our CSD way.
- Explain using diagrams and flowcharts how to write the signal Lamp. Explain the ISR().
- Replace the external CLK signal by the internal TMRO.

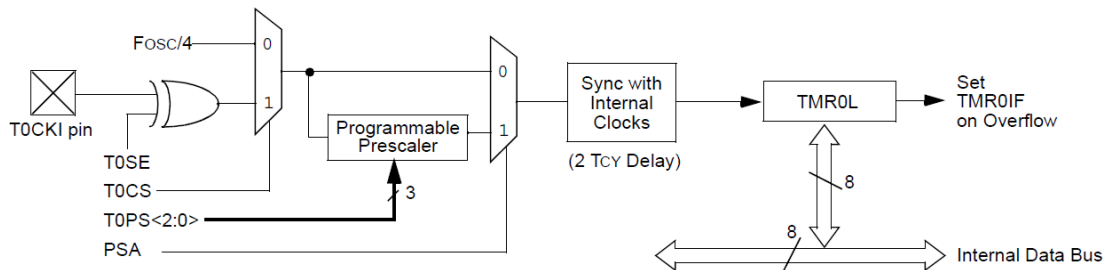

**REGISTER 11-1: T0CON: TIMER0 CONTROL REGISTER**

R/W-1	R/W-1	R/W-1	R/W-1	R/W-1	R/W-1	R/W-1	R/W-1
TMR0ON	T08BIT	T0CS	T0SE	PSA	T0PS2	T0PS1	T0PS0
bit 7							bit 0

Legend:			
R = Readable bit	W = Writable bit	U = Unimplemented bit, read as '0'	
-n = Value at POR	'1' = Bit is set	'0' = Bit is cleared	x = Bit is unknown

- bit 7 **TMR0ON:** Timer0 On/Off Control bit  
1 = Enables Timer0  
0 = Stops Timer0
- bit 6 **T08BIT:** Timer0 8-Bit/16-Bit Control bit  
1 = Timer0 is configured as an 8-bit timer/counter  
0 = Timer0 is configured as a 16-bit timer/counter
- bit 5 **T0CS:** Timer0 Clock Source Select bit  
1 = Transition on T0CKI pin  
0 = Internal instruction cycle clock (CLKO)
- bit 4 **T0SE:** Timer0 Source Edge Select bit  
1 = Increment on high-to-low transition on T0CKI pin  
0 = Increment on low-to-high transition on T0CKI pin
- bit 3 **PSA:** Timer0 Prescaler Assignment bit  
1 = Timer0 prescaler is not assigned. Timer0 clock input bypasses prescaler.  
0 = Timer0 prescaler is assigned. Timer0 clock input comes from prescaler output.
- bit 2-0 **T0PS<2:0>:** Timer0 Prescaler Select bits  
111 = 1:256 Prescale value  
110 = 1:128 Prescale value  
101 = 1:64 Prescale value  
100 = 1:32 Prescale value  
011 = 1:16 Prescale value  
010 = 1:8 Prescale value  
001 = 1:4 Prescale value  
000 = 1:2 Prescale value

Fig. 5. TMR0. Hardware block diagram and configuration bits from Microchip datasheet.

**Problem 5. Earbuds touch-button controller**

Design the button decoder (*Button\_controller*) typical in many tactile or touch commercial Bluetooth earbuds. The idea is to assign a binary function code FC(1..0) depending on the clicks detected. Fig. 6 shows typical waveforms for commercial earbuds when the user is touching the button pad. A convenient sampling frequency is  $f_{CLK} = 8$  Hz.

- When no clicks are detected FC = "00". It means that the system is Idle.
- When one short click is detected, it means audio volume up. The function code value assigned is FC = "01".
- When two consecutive short clicks are detected, it means alternatively play/pause. The function codes assigned are FC = "10" / "11".

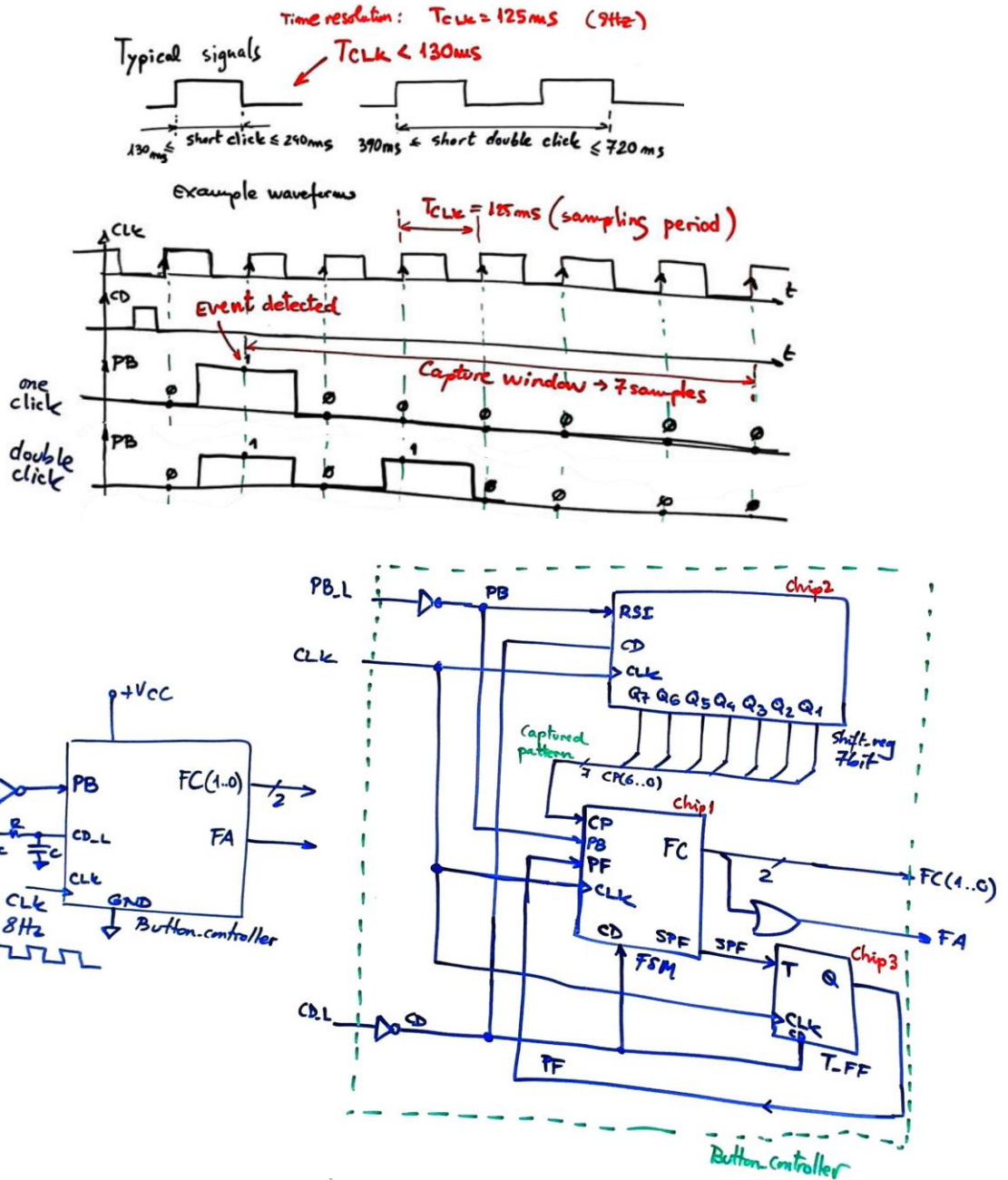



Fig. 6. Click waveforms, symbol and proposed internal schematic for the earbud controller.

**Section 1. Hardware design (FPGA, VHDL).**

- Explain the circuit in Fig. 6. Why it may work for capturing click events and obtaining the function codes? Why a captured pattern CP(6..0) of seven push-button samples is ok to identify click events?
- Propose the FSM state diagram.
- Draw the FSM structure. Draw the state register schematic using *D\_FF*. Code the internal states in one-hot. How many VHDL files are required to solve this plan C2 project?
- Propose the CC1 and CC2 truth tables and their flowcharts.
- Design a *CLK\_Generator* circuit to obtain the 8 Hz sampling frequency from a 26 MHz crystal oscillator. How many *D\_FF* will contain the full *Button\_controller* design?

**Section 2. Microcontroller design.**

- f) Draw a schematic to implement the *Button\_controller* using a PIC18F4520 microcontroller. Represent the power-on reset (MCLR\_L) circuit and explain how it works. Draw the oscillator circuit using a 12 MHz quartz crystal.
- g) Adapt the state diagram so that it can be driven by interrupt flags. Do the interrupts have to be enabled all the time?
- h) Draw the hardware-software diagram indicating the required RAM variables and how the FSM and sampling operations for capturing the PB signal is solved in software. Organise the main program as a FSM in our CSD way.
- i) Explain using diagrams and flowcharts how to write FC(1..0). Explain the ISR().
- j) Replace the external CLK signal by the internal TMR2 so that the PB signal is sampled at the same 8 Hz frequency. Configure the TMR2 parameters and explain the idea why such peripheral can be for this purpose.

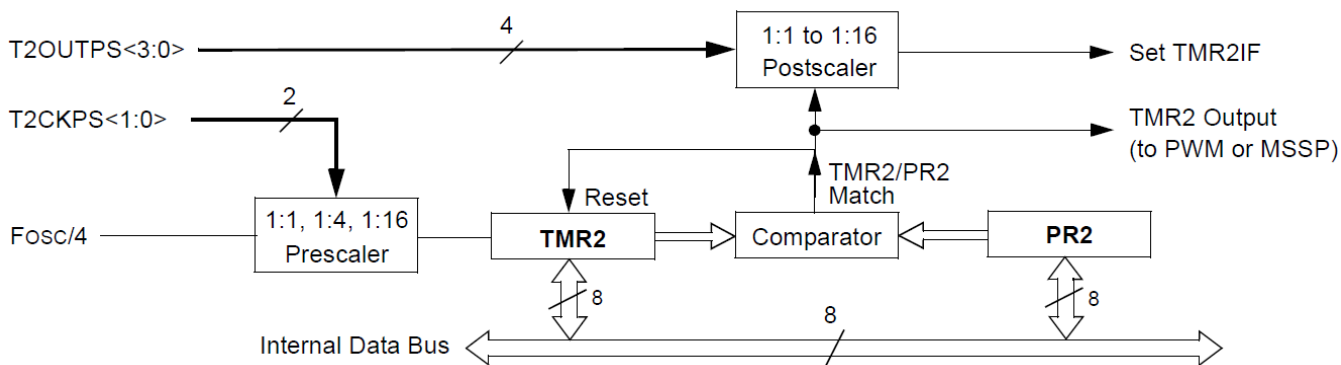

**REGISTER 13-1: T2CON: TIMER2 CONTROL REGISTER**

U-0	R/W-0	R/W-0	R/W-0	R/W-0	R/W-0	R/W-0	R/W-0
—	T2OUTPS3	T2OUTPS2	T2OUTPS1	T2OUTPS0	TMR2ON	T2CKPS1	T2CKPS0
bit 7							bit 0

**Legend:**  
 R = Readable bit      W = Writable bit      U = Unimplemented bit, read as '0'  
 -n = Value at POR      '1' = Bit is set      '0' = Bit is cleared      x = Bit is unknown



- bit 7      **Unimplemented:** Read as '0'
- bit 6-3      **T2OUTPS<3:0>:** Timer2 Output Postscale Select bits  
 0000 = 1:1 Postscale  
 0001 = 1:2 Postscale  
 •  
 •  
 •  
 1111 = 1:16 Postscale
- bit 2      **TMR2ON:** Timer2 On bit  
 1 = Timer2 is on  
 0 = Timer2 is off
- bit 1-0      **T2CKPS<1:0>:** Timer2 Clock Prescale Select bits  
 00 = Prescaler is 1  
 01 = Prescaler is 4  
 1x = Prescaler is 16

Fig. 7. TMR2 block diagram from Microchip datasheet.
 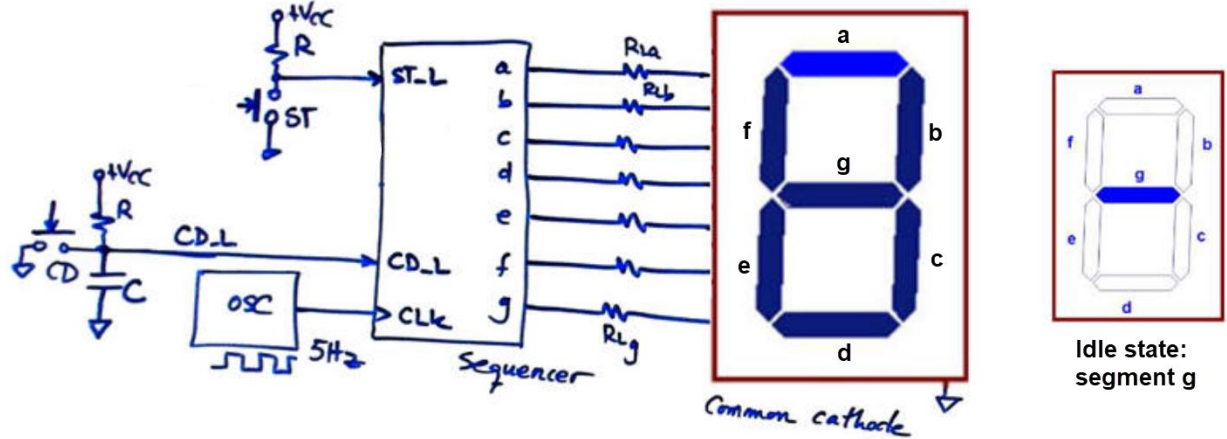
### Problem 6. Sequencer for a 7-segment display

We want to design a driver to show a LED sequence that indicates a kind of clockwise movement in a single 7-segment display. Fig. 8 represents the symbol, the 7-segment sequence and the proposed schematic diagram of the application. CLK signal to move segments is a 5 Hz rectangular wave.

- When clicking the active-low push-button start/stop (ST\_L) the system start running continuously generating the indicated LED sequence.
- When running, if ST\_L is clicked again, the system stops **after** completing the sequence.



CD-L =  $\overline{\text{CD}}$  → Asynchronous reset  
 ST-L =  $\overline{\text{ST}}$  → Start running when idle, stop when running after completing the sequence

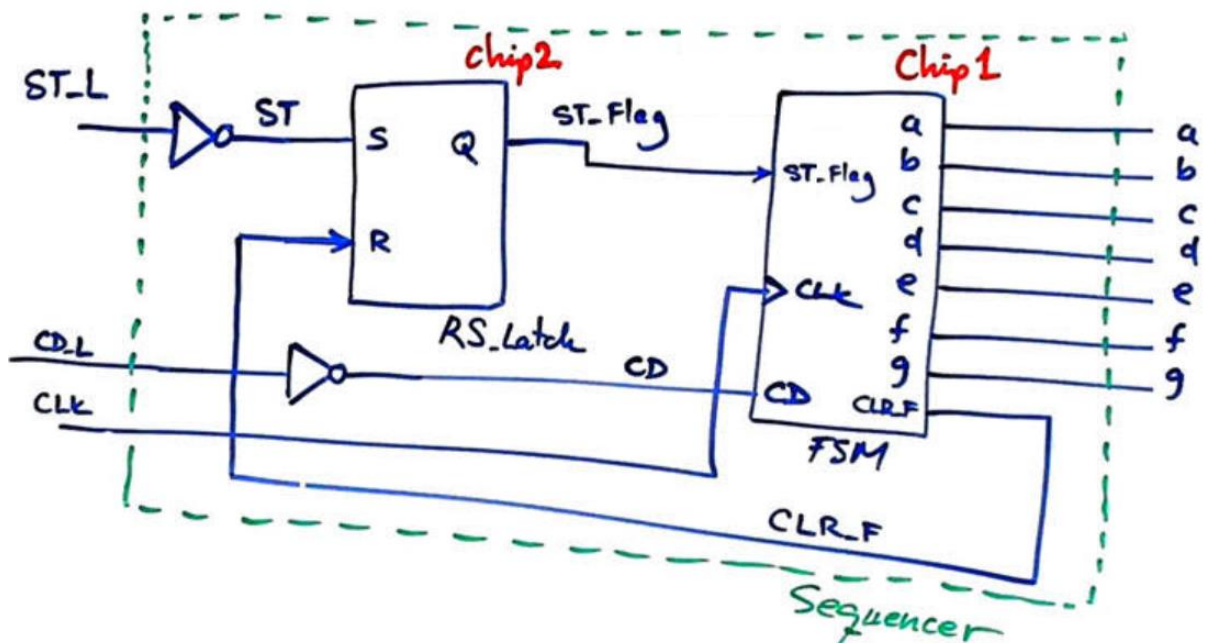


Fig. 8. Sequencer symbol, LED pattern generated in the 7-segment display and proposed schematic.

**Section 1.** Hardware design (FPGA, VHDL).

- a) Explain the circuit in Fig. 8. Why it may work for sequencing LED and for controlling the push-button. How the stop flag is generated and memorised?
  - b) Propose the FSM state diagram.
  - c) Draw the FSM structure. Draw the state register schematic using  $D\_FF$ . Code the internal states in binary sequential (radix-2). How many VHDL files are required to solve this plan C2 project?
  - d) Propose the CC1 and CC2 truth tables and their flowcharts.
  - e) Design a  $CLK\_Generator$  circuit to obtain the 5 Hz sampling frequency from a 26 MHz crystal oscillator. How many  $D\_FF$  will contain the full *Sequencer* design?
- 

**Section 2.** Microcontroller design.

- f) Draw a schematic to implement the *Sequencer* using a PIC18F4520 microcontroller. Draw the power-on reset (MCLR\_L) circuit and explain how it works. Draw the oscillator circuit using a 12 MHz quartz crystal.
- g) Adapt the state diagram so that it can be driven by interrupt flags. Do the interrupts have to be enabled all the time?
- h) Draw the hardware-software diagram indicating the required RAM variables and how the FSM is solved in software. Organise the main program as a FSM in our CSD way.
- i) Explain using diagrams and flowcharts how to write the segment signals a, b, c, d, e, f and g. Explain the ISR().
- j) Replace the external CLK signal by the internal TMRO (represented above in Fig. 5). Configure the TMRO parameters and explain the idea why such peripheral can be for this purpose.