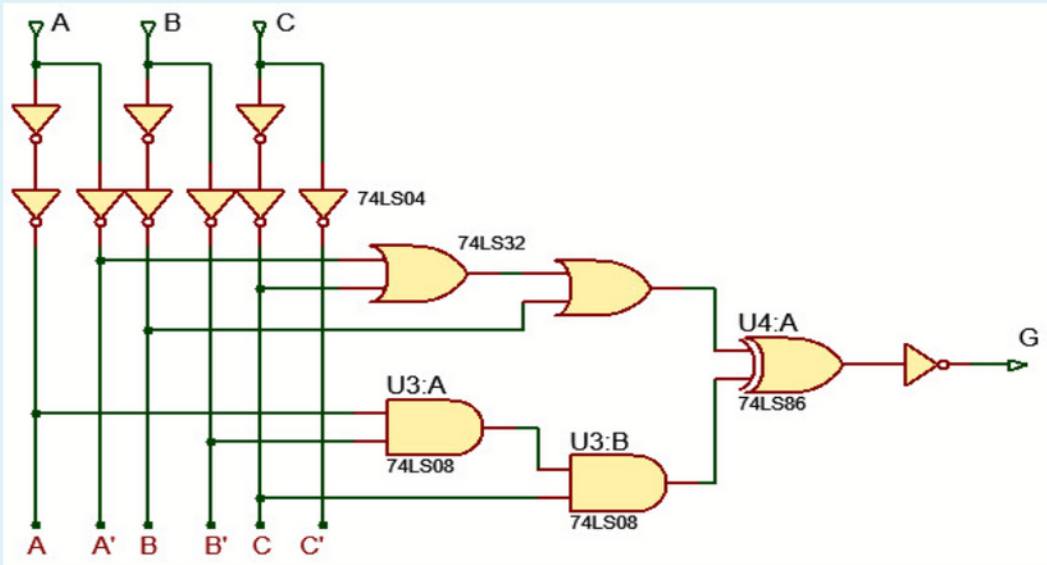


## Sample questions for projects P1- P2 - P3 - P4

Analyse the circuit in the picture and deduce the output  $G = f(A, B, C)$ .



Select one:

- a.  $G = (A' + B + C) \oplus (AB'C)$
- b.  $G = ((A' + B + C) \cdot (A' + B + C') + (A' + B + C)' \cdot (AB'C))'$
- c.  $G = ((A + B' + C') \cdot (AB'C)' + (A' + B' + C)' \cdot (AB'C))'$

For a boolean function of  $n$  variables  $x_1, \dots, x_n$ , a sum term in which each of the  $n$  variables appears **once** (in either its complemented or uncomplemented form) is called a **maxterm**.


A single maxterm  $n$  gives a '0' value for just one combination of the input variables. Thus, it is possible to write the truth table of a logical function as a product of maxterms.

Select one:
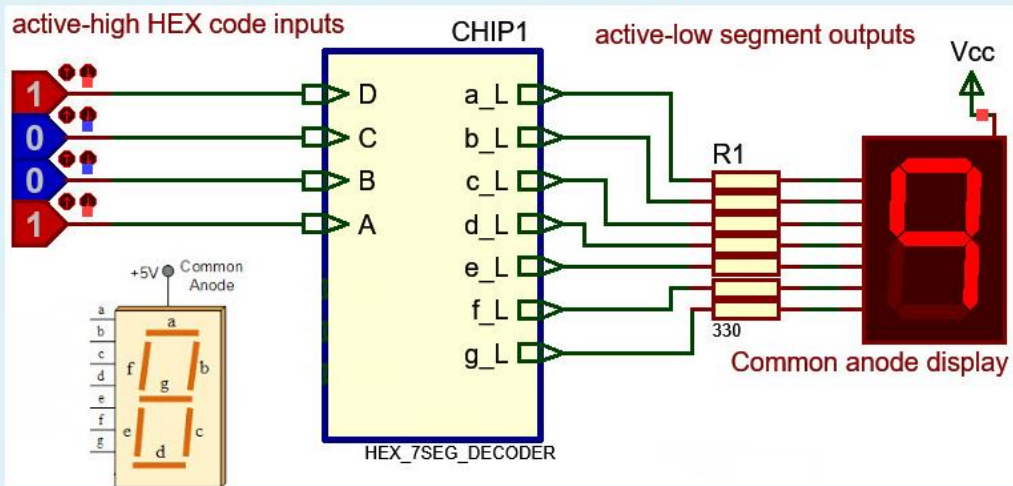
### Answers

- True
- False

This circuit is a hexadecimal to seven-segment decoder which has active-low outputs. The number '9' is represented. Which is the value of the output vector  $[a_L, b_L, c_L, \dots, g_L]$ ?



Select one:

- a. [1 1 1 0 0 1 1]
- b. [1 1 1 0 0 1 0]
- c. [0 0 0 1 1 0 1]
- d. [0 0 0 1 1 0 0]

The picture shows the truth table resulting from the WolframAlpha numerical engine when ordered to obtain it. The function is described as:  $P = f(D1, D0, A, B)$  Thus, find the sum of minterms.


Truth table:

A	B	D0	D1	P
T	T	T	T	T
T	T	T	F	T
T	T	F	T	F
T	T	F	F	F
T	F	T	T	F
T	F	T	F	T
T	F	F	T	T
T	F	F	F	T
F	T	T	T	F
F	T	T	F	F
F	T	F	T	T
F	T	F	F	T
F	F	T	T	T
F	F	T	F	F
F	F	F	T	F
F	F	F	F	T

Select one:

 - a.  $P = f(D1, D0, A, B) = \sum m(0, 1, 2, 6, 7, 9, 10, 12, 15)$
- b.  $P = f(D1, D0, A, B) = \sum M(3, 4, 5, 8, 11, 13, 14)$
- c.  $P = f(D1, D0, A, B) = \sum m(0, 1, 5, 6, 7, 10, 11, 12, 15)$

This circuit is build using gates of the HCT (High Speed CMOS) technology that has the characteristics given below. Which statement is false?



**DC Electrical Specification**

**V<sub>CC</sub> = 4.5 V**

PARAMETER	SYMBOL	25°C			UNITS
		MIN	TYP	MAX	
<b>HC TYPES</b>					
High Level Input Voltage	V <sub>IH</sub>	3.15	-	-	V
Low Level Input Voltage	V <sub>IL</sub>	-	-	1.35	V
High Level Output Voltage	V <sub>OH</sub>	4.4	-	-	V
Low Level Output Voltage	V <sub>OL</sub>	-	-	0.1	V


Select one:

- a.  $V_{IL\ max}$  is the maximum voltage that can understand  $V_{i2}$  as a logic '0'
- b. In good operation conditions, when generating a low '0',  $V_{O1}$  can be higher that  $V_{OL\ max} = 0.1\ V$
- c. If  $V_{O1}$  is below the the  $V_{OH\ min} = 4.4\ V$  the next gate input voltage  $V_{i2}$  may not understand it as a valid '1' .
- d. If the NAND gate is operating correctly, when generating an output level '1',  $V_{O1}$  is always above the the threshold  $V_{OH\ min} = 4.4\ V$

Running the EDA VHDL simulator and examining the output timing diagram we can determine the truth table of a given circuit. For instance, in the capture below, we measure that:

$$K = f(D1, D0, A, B) = K(1100) = \mathbf{0} \rightarrow M_{12}$$

$$K(1001) = \mathbf{1} \rightarrow m_9$$

 


Select one:
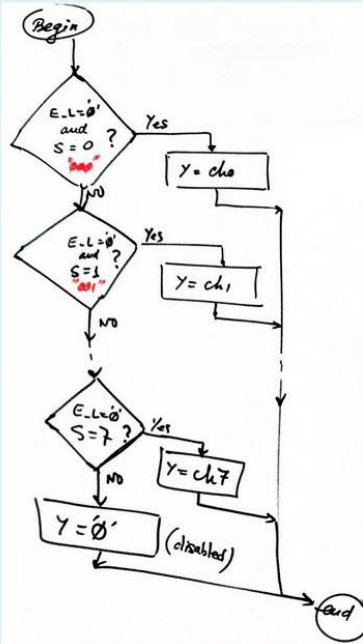
## Answers

- True
- False

We plan a VHDL behavioural description of a **MUX\_8** as shown in the flow chart sketch below. We have found up to three possible circuits to **copy & adapt** from the *digsys* web belonging to MUX\_4 projects. Which is preferred one?



Select one:

a.

```
SIGNAL X_in : STD_LOGIC_VECTOR (5 downto 0);
BEGIN
  Y <= '0' when std_match(X_in,"00---0") and E_L = '0' else
        '1' when std_match(X_in,"00---1") and E_L = '0' else
        '0' when std_match(X_in,"01--0") and E_L = '0' else
        '1' when std_match(X_in,"01--1") and E_L = '0' else
        '0' when std_match(X_in,"10-0--") and E_L = '0' else
        '1' when std_match(X_in,"10-1--") and E_L = '0' else
        '0' when std_match(X_in,"110---") and E_L = '0' else
        '1' when std_match(X_in,"111---") and E_L = '0' else
        '0';

  -- Extra logic (simple buffers in this case)

  X_in(5) <= S(1);
  X_in(4) <= S(0);
  X_in(3) <= Ch3;
  X_in(2) <= Ch2;
  X_in(1) <= Ch1;
  X_in(0) <= Ch0;
```


c.

```
BEGIN
  PROCESS ( E_L, S, Ch3,Ch2,Ch1,Ch0)
  BEGIN
    IF E_L = '1' THEN
      Y <= '0'; -- disable
    ELSE
      IF S = "00" THEN y <= Ch0;
      ELSIF S = "01" THEN y <= Ch1;
      ELSIF S = "10" THEN y <= Ch2;
      ELSE y <= Ch3;
      END IF ;
    END IF ;
  END PROCESS;
END truth_table;
```

b.

```
architecture truth_table of MUX_4 is
begin
  y <= Ch0 when (s = "00" and E_L = '0') else
        Ch1 when (s = "01" and E_L = '0') else
        Ch2 when (s = "10" and E_L = '0') else
        Ch3 when (s = "11" and E_L = '0') else '0';
end truth_table;
```

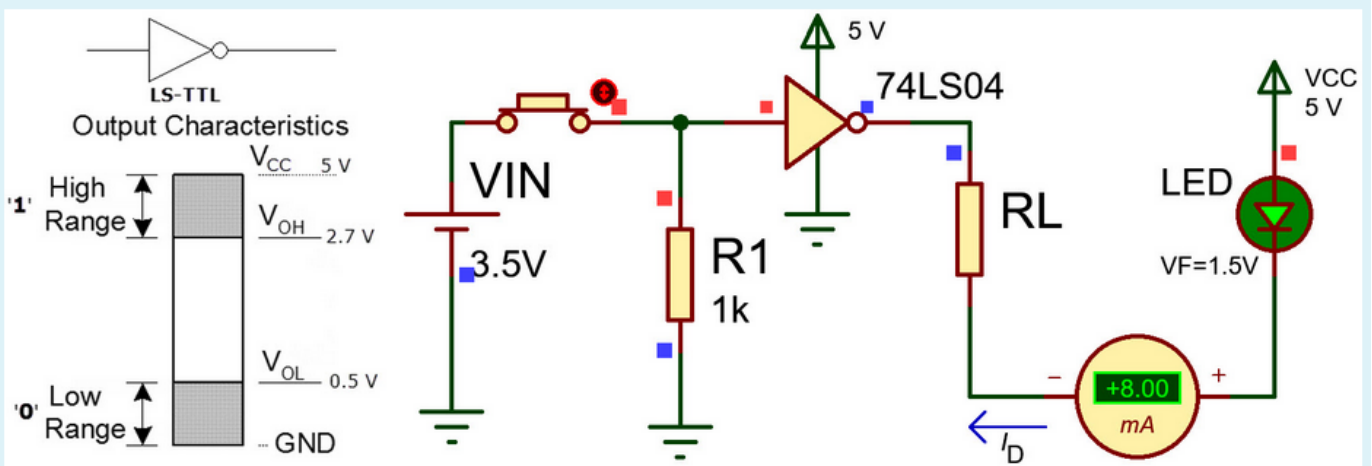
Which is the value of the limiting resistor  $R_L$  that bias the LED with  $I_D = 8\text{mA}$  in the worst case scenario?



Select one:

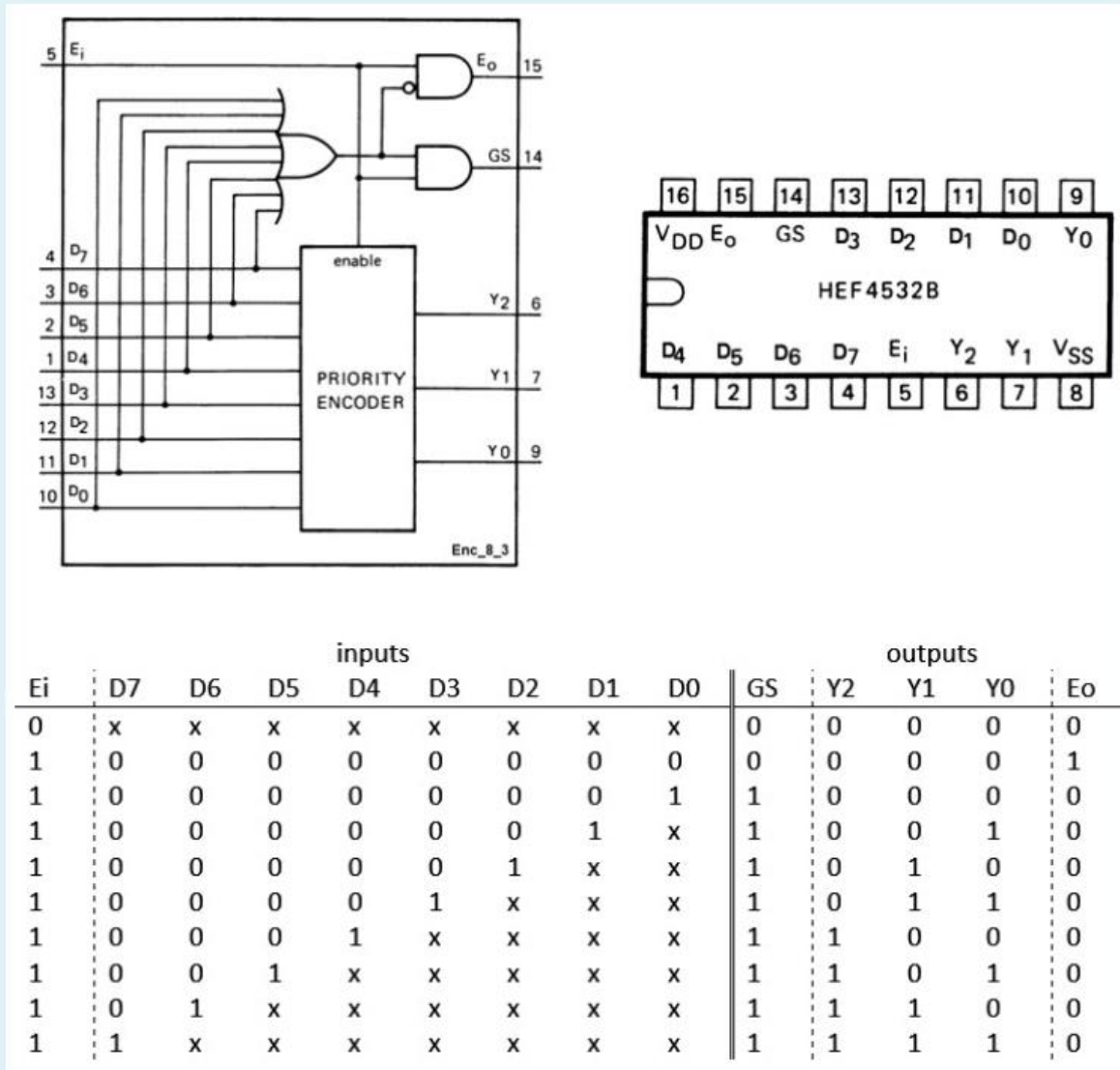- a.  $R_L = 375 \Omega$
- b.  $R_L = 150 \Omega$
- c.  $R_L = 437.5 \Omega$


This is a HEF4532B, a commercial encoder 8 to 3 with priority high. How many minterms have the outputs GS and Y0?



Select one:

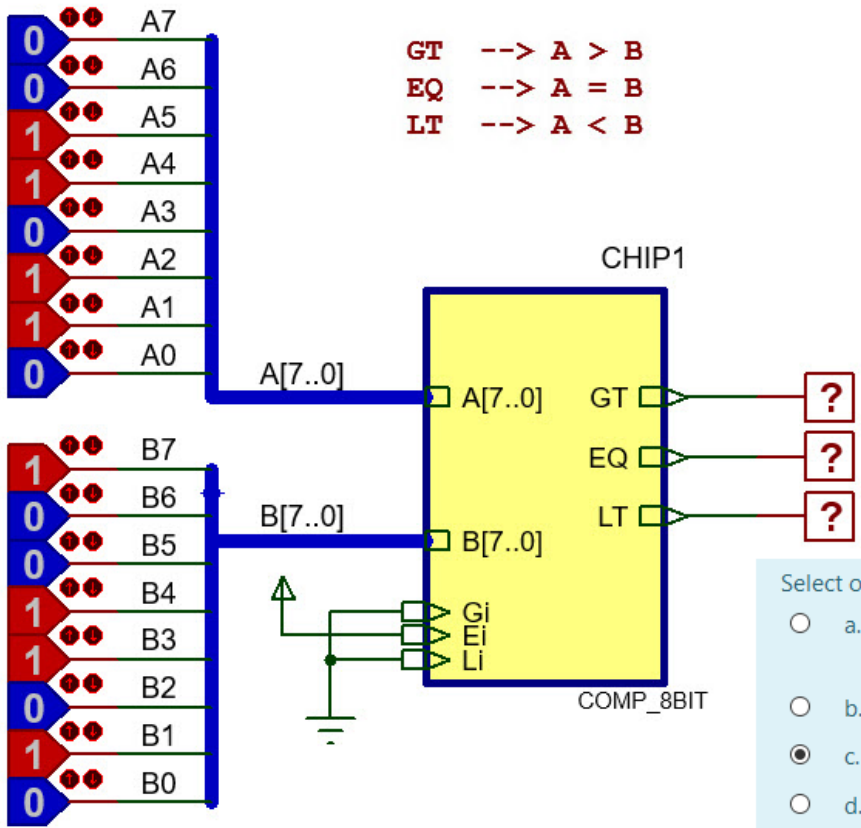- a. **GS** has 8 minterms and **Y0** has 6 minterms.
- b. **GS** has 255 minterms and **Y0** has 170 minterms.
- c. **GS** has 2 minterms and **Y0** has 6 minterms.


The circuit in the picture is a *Comp\_8bit*, a comparator of radix-2 binary numbers. Which is the output of the circuit when driven by these input vectors?



Select one:

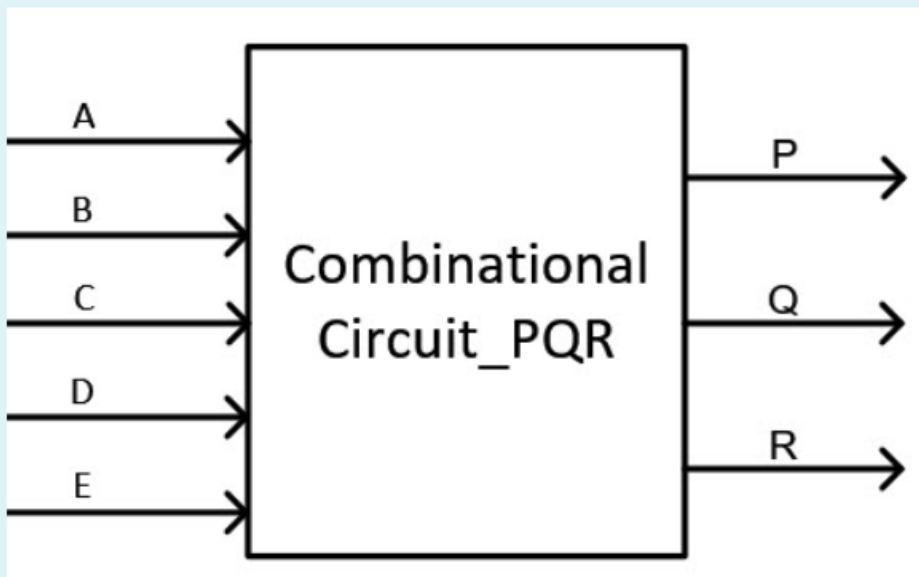- a. GT = '1'; EQ = '0'; LT = '0'
- b. GT = '1'; EQ = '1'; LT = '0'
- c. GT = '0'; EQ = '0'; LT = '1'
- d. GT = '0'; EQ = '1'; LT = '0'


The *Circuit\_PQR* in the picture is planned on the method of decoders, and the decoder is build internally chaining 4 components *DEC\_3\_8*. How many VHDL files will contain this hierarchical structural project?



Select one:

 - a. 6 VHDL files
- b. 4 VHDL files
- c. 1 VHDL files
- d. 3 VHDL files

The circuit below is a 3-bit odd-parity generator solved using the method of multiplexers and a MUX\_8. Furthermore, the MUX\_8 component is build internally using MUX\_2. The resulting  $Y_{OP} = f(X_2, X_1, X_0)$  is faster (less propagation delay) than the circuit produced using maxterms  $Y_{OP} = f(X_2, X_1, X_0) = \prod\{0, 3, 5, 6\}$




Select one:

Answers

- True
- False

The step number 4 in this design flow, the functional simulation, allows you to measure gate delays, propagation times and the worst case scenario to deduce the maximum frequency of operation of the designed circuit.
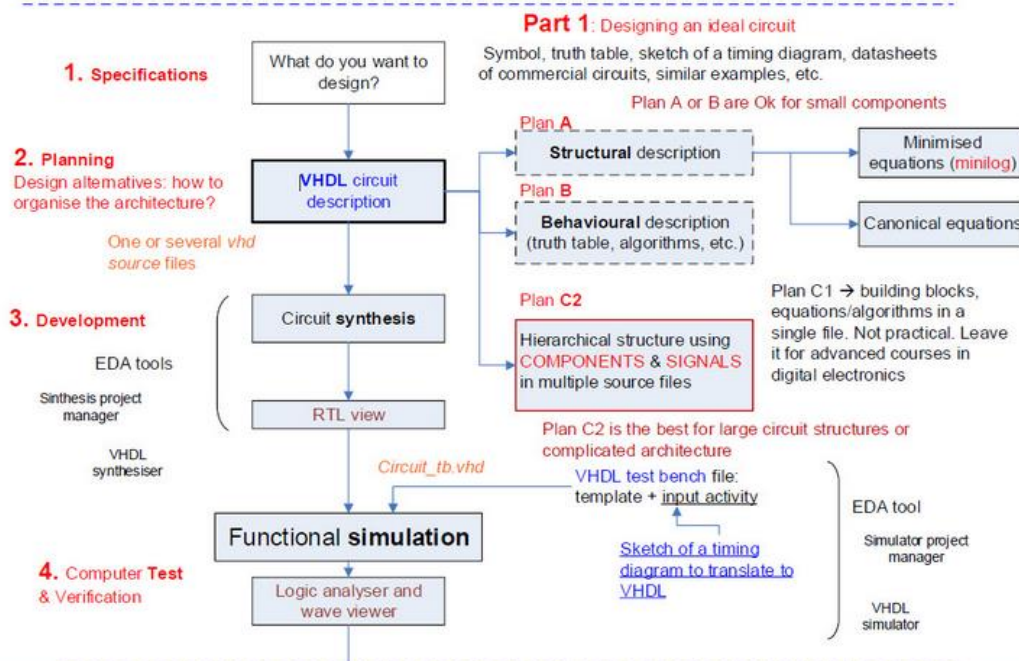
### VHDL design flow for digital circuits (flat / hierarchical architectures)




Select one:

Answers

- True
- False




Which is the output of the circuit ?

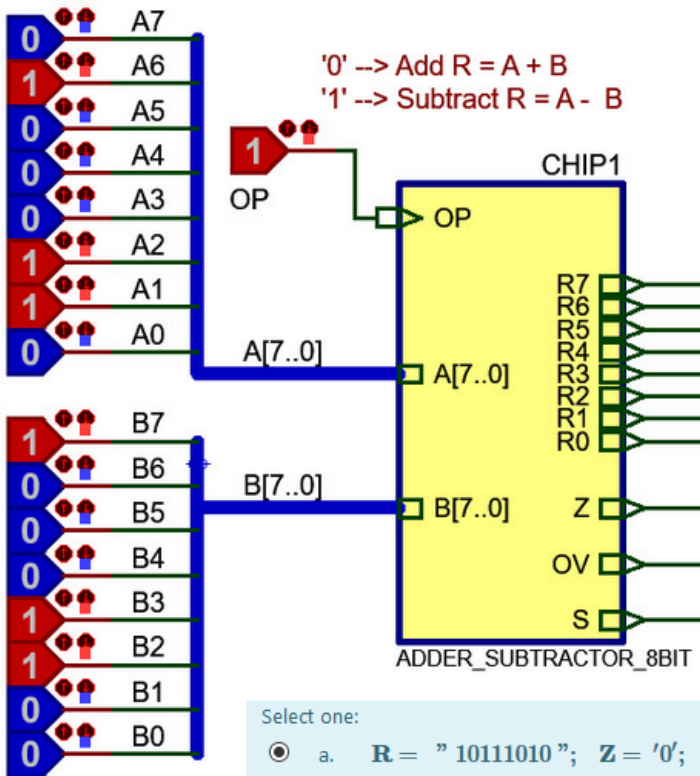

Select one:

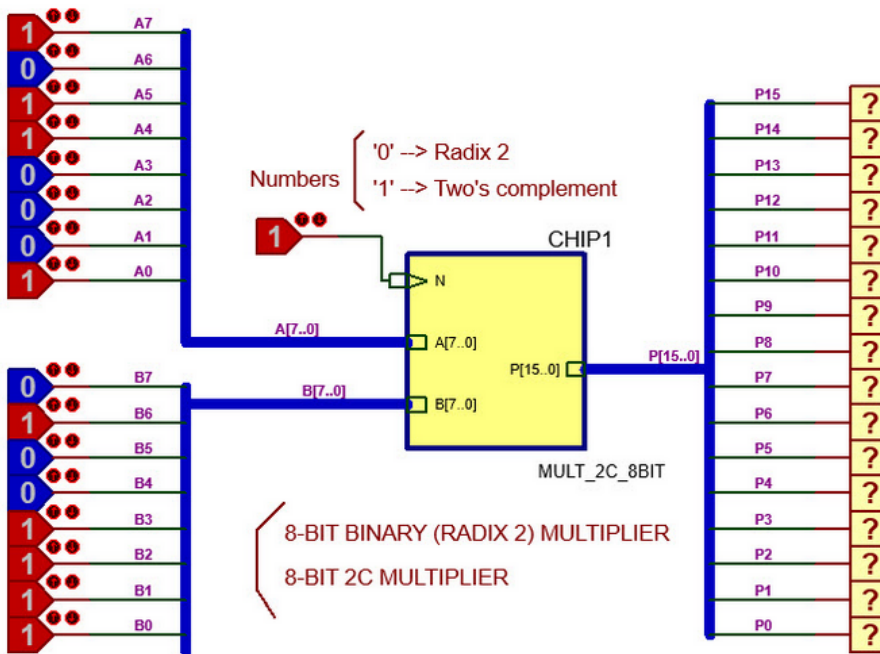- a. **R = " 10111010 "; Z = '0'; OV = '1'; S = '1'**
- b. **R = " 01000101 "; Z = '0'; OV = '0'; S = '0'**
- c. **R = " 10111010 "; Z = '0'; OV = '0'; S = '1'**


The circuit in the picture is a *Mult\_2C\_8bits*, a binary multiplier that has a control input **N** to operate with radix 2 data when **N = 0**, and with two's complement data when **N = 1**. Which is the output of the circuit when driven by these input vectors?



Select one:

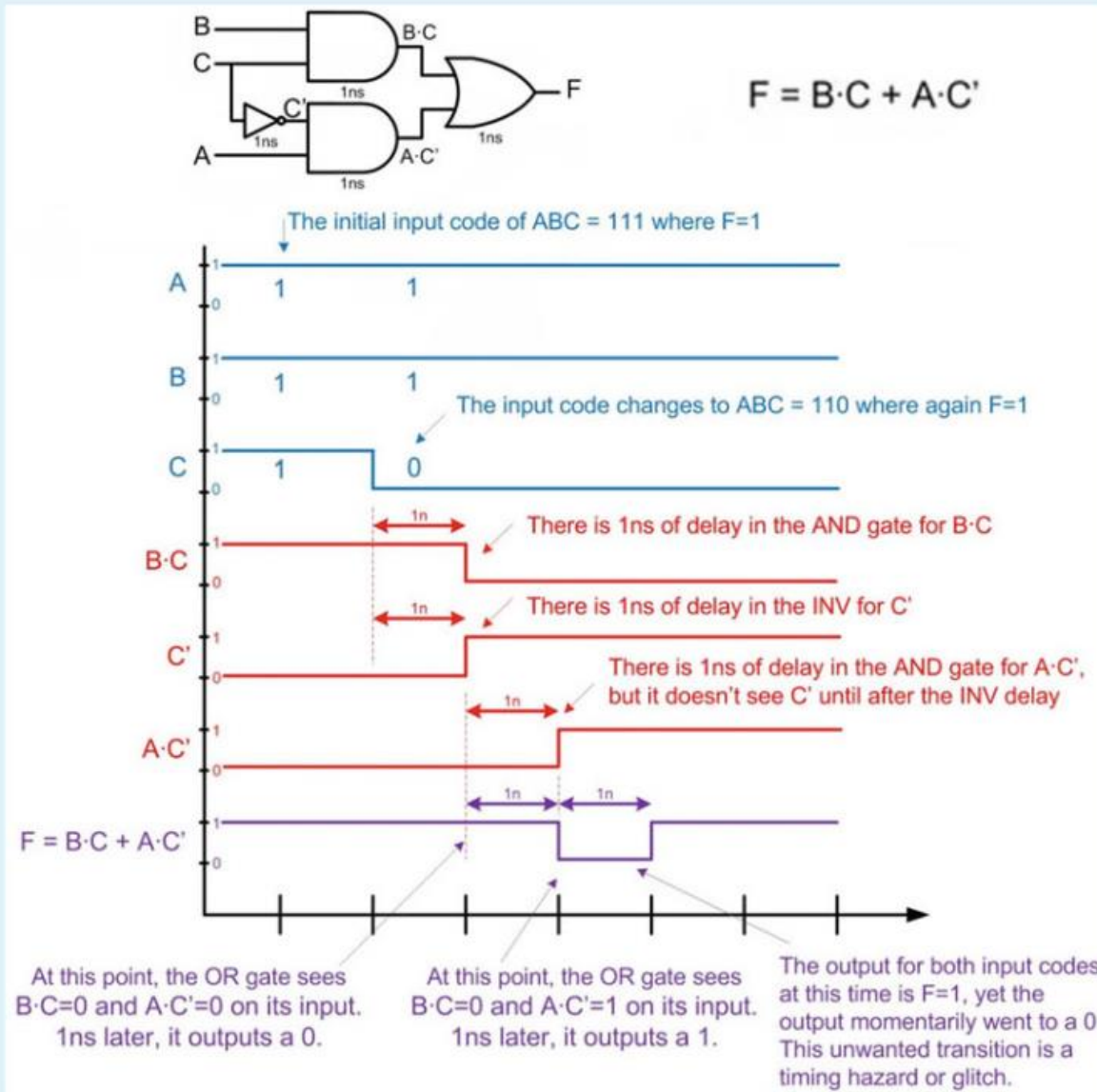- a. **P(15..0) = " 1110 0111 1001 1111 "**
- b. **P(15..0) = " 1001 1111 0111 1111 "**
- c. **P(15..0) = " 0011 0110 1001 1111 "**


Timing hazards or glitches refer to unwanted transitions on the output of a combinational logic circuit. These are most commonly due to different delay paths through the gates in the circuit. In real circuitry there is always a finite propagation delay through each gate. Consider the circuit analysed below where a timing diagram shows signal transitions and hand-made annotations.



Select one:

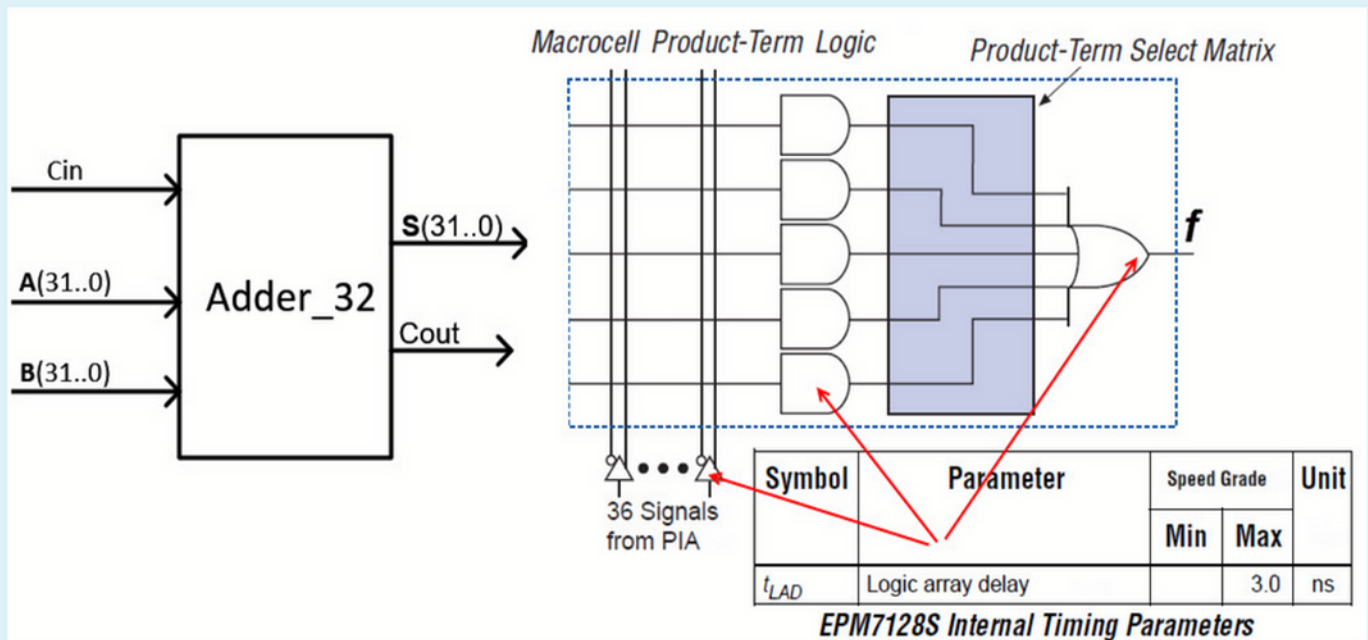- a. Using VHDL test benches we can measure the circuit's delay such as here (3 ns) using the functional simulation EDA tool.
- b. Using VHDL test benches we can measure the circuit's delay such as here (3 ns) using the gate-level simulation EDA tool.
- c. Using VHDL test benches we can measure the circuit's delay such as here (2 ns) using the gate-level simulation EDA tool.
- d. Using VHDL test benches we can measure the circuit's delay such as here (2 ns) using the functional simulation EDA tool.

The *Adder\_32* entity in the picture is based on the ripple-carry technique of 32 *Adder\_1bit* cells, which internally are structured using 3-levels-of-logic gates as shown in the simplified macrocell. The entity is implemented in an Intel-Altera CPLD MAX7128S chip showing the characteristics in the table. Calculate the propagation delay and the maximum speed of operation.



Select one:

- a.  $t_P = 96 \text{ ns}; f_{max} = 10.4 \text{ MHz}$
- b.  $t_P = 288 \text{ ns}; f_{max} = 1.73 \text{ MHz}$
- c.  $t_P = 3 \text{ ns}; f_{max} = 333.3 \text{ MHz}$