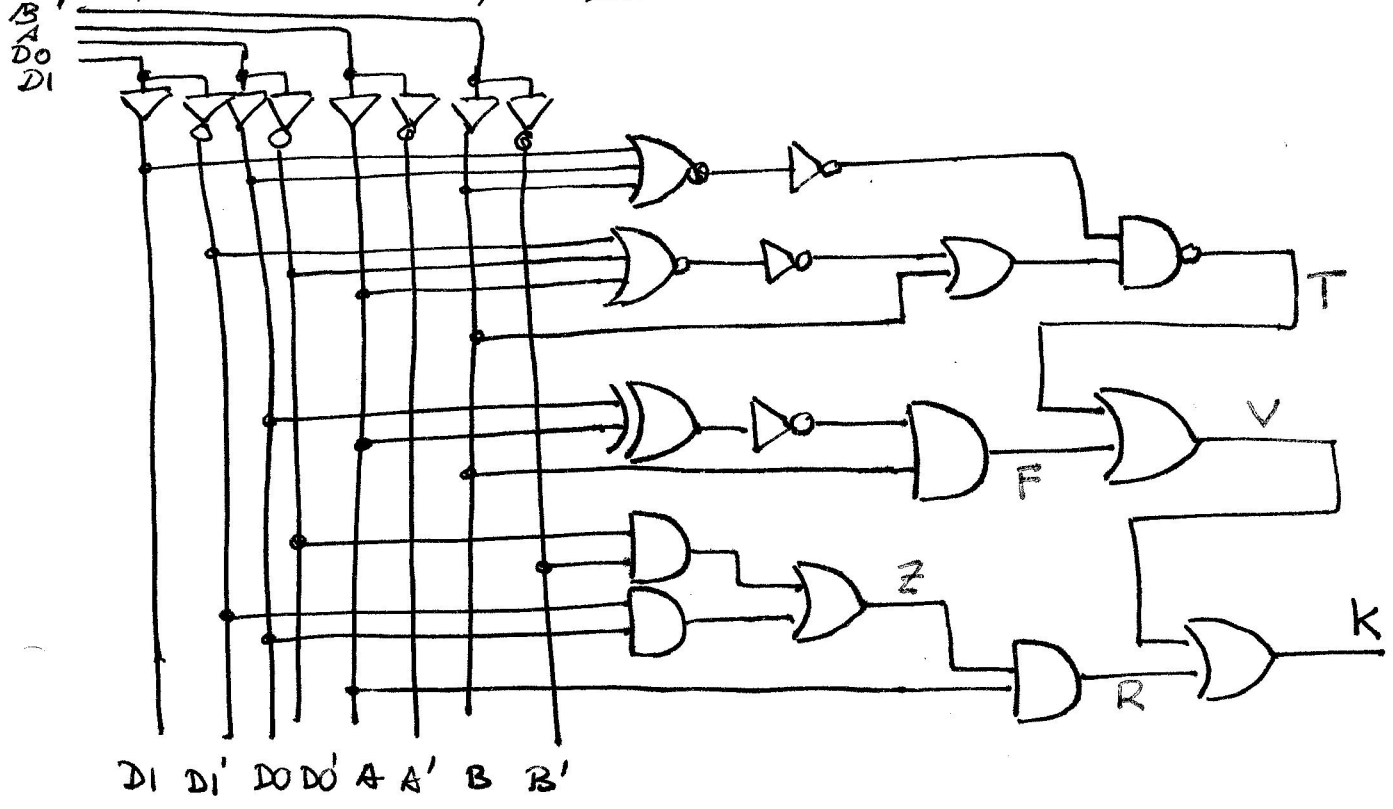


1 Specifications: Analyse Circuit-K




⇒ Find circuit's truth table using a pen-and-paper method (1)


$$K = f(D_1, D_0, A, B)$$

2. Plan (Method 1) analyse section by sections

2

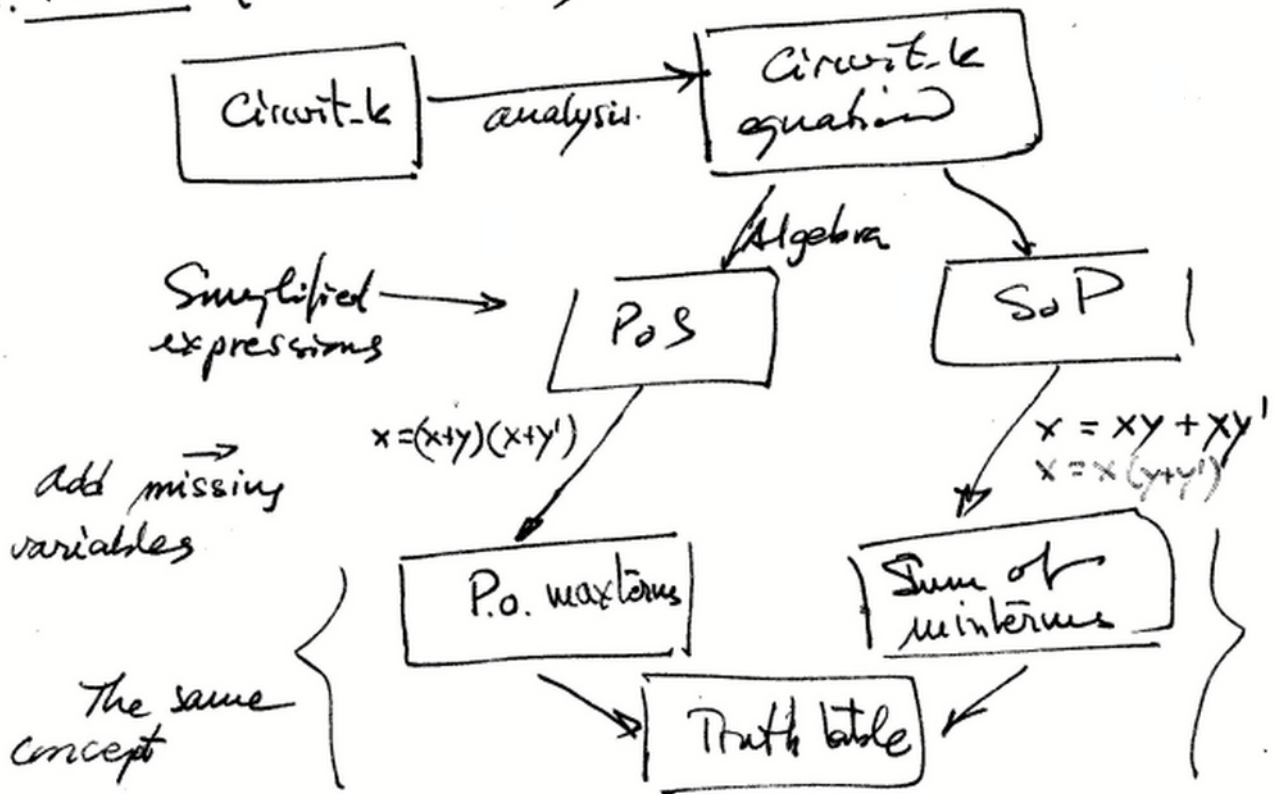

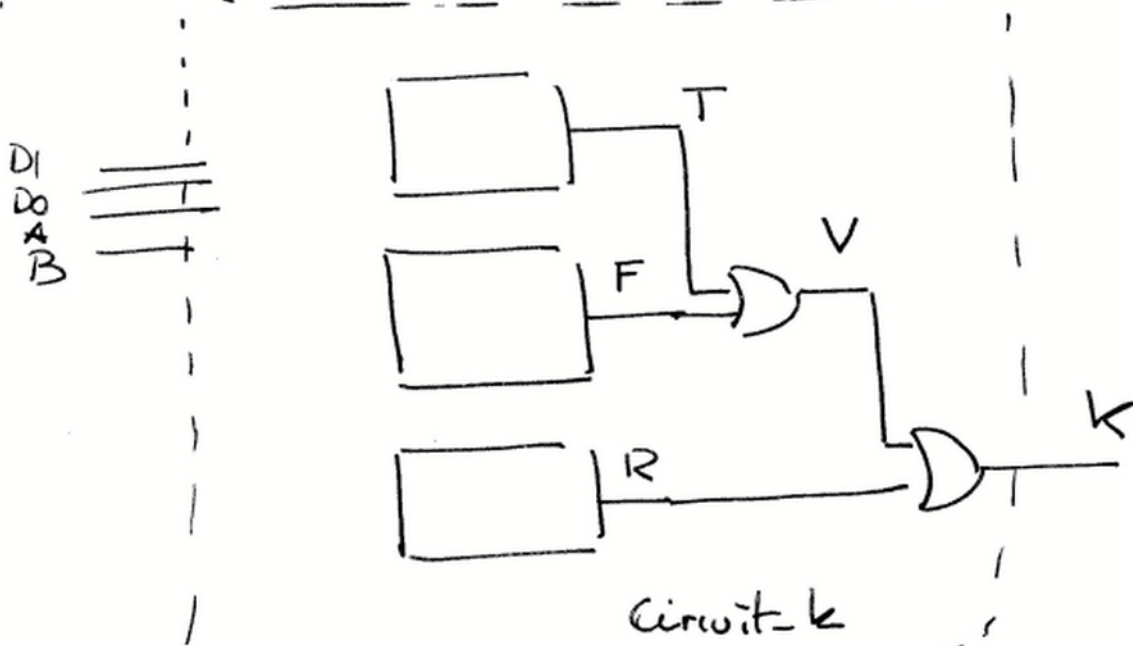→ This is the idea of solving it using smaller circuit sections



$$K = R + V = R + (F + T)$$

3. Development

3

1. Find circuit's general equation

Naming wires:

$$K = f(D_1, D_0, A, B) = R + V$$

OR
↓
↑

$$\overline{T} + F = V$$

A · Z

$$Z = \left[(D_0' \cdot B') + (D_1' \cdot D_0) \right]$$

$$F = (D_0 \oplus A)' \cdot B$$


$$T = \left[\left[\left((D_1' + D_0' + A)' \right)' + B \right] \cdot \left((D_1 + D_0 + B)' \right)' \right]'$$

↑
AND

$$K = \left[\left[\left((D_1' + D_0' + A)' \right)' + B \right] \cdot \left((D_1 + D_0 + B)' \right)' \right]' + B \cdot (D_0 \oplus A)' + A \left((D_0' \cdot B') + (D_1' \cdot D_0) \right)$$

This equation is the same as the circuit-k representation

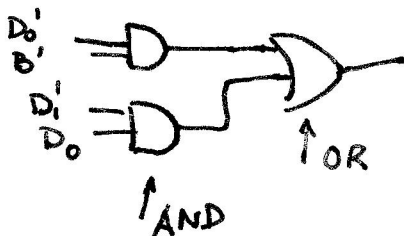For instance: $(D_0' \cdot B') + (D_1' \cdot D_0)$



Simplification term by term

$$\left(\underbrace{(D_1' + D_0' + A + B)}_x \cdot \underbrace{(D_1 + D_0 + B)}_y \right)' + B \underbrace{(D_0 A' + D_0' A)}_{\text{XOR}} + A \cdot D_0' \cdot B' + A D_1' D_0 =$$

$$\left(x \cdot y \right)' = x' + y' \quad \left(\rightarrow \text{De Morgan's Law} \right)$$

$$\left(x + y \right)' = x' \cdot y'$$

$$= (D_1' + D_0' + A + B)' + (D_1 + D_0 + B)' + B (D_0 A')' \cdot (D_0' A)' + A D_0' B' + A D_1' D_0 =$$

$$= D_1'' \cdot D_0'' \cdot A' \cdot B' + D_1' \cdot D_0' \cdot B' + B ((D_0' + A) \cdot (D_0 + A')) + A D_0' B' + A D_1' D_0 =$$

$$= D_1' \cdot D_0' \cdot A' \cdot B' + D_1' D_0' B' + B \left(\underset{\downarrow 0'}{D_0' D_0} + \underset{\downarrow 0'}{D_0' A'} + A D_0 + A A' \right) + A D_0' B' + A D_1' D_0$$

$$K = D_1' D_0' A' B' + D_1' D_0' B' + B D_0' A' + B A D_0 + A D_0' B' + A D_1' D_0$$

K = is a sum of six products

SoP

adding missing variables

Now, let's convert products into minterms

$$x = x(y + y')$$

$$xy + xy'$$

$$D_1 D_0 A' B' \rightarrow \text{min terms } m_{1100} = m_{12}$$

$$D_1' D_0' B' = D_1' D_0' B' (A + A') = D_1' D_0' B' A + D_1' D_0' B' A'$$

reorder variables $\Rightarrow D_1' D_0' A B' + D_1' D_0' A' B'$

$$m_{0010} + m_{0000}$$

$$m_2 + m_0$$

And so, in the same way all the other terms (products)

$$B D_0' A' = (D_1 + D_1') D_0' A' B = D_1 D_0' A' B + D_1' D_0' A' B$$

$$\hookrightarrow m_9 + m_1$$

$$m_{1001} + m_{0001}$$

$$B A D_0 = (D_1 + D_1') D_0 A B = D_1 D_0 A B + D_1' D_0 A B$$

$$\hookrightarrow m_{15} + m_7$$

$$m_{1111} + m_{0011}$$

$$A D_0' B' = (D_1 + D_1') D_0' A B' = D_1 D_0' A B' + D_1' D_0' A B'$$

$$\hookrightarrow m_{10} + m_2$$

$$m_{1010} + m_{0010}$$

$$A D_1' D_0 = D_1' D_0 A (B + B') = D_1' D_0 A B + D_1' D_0 A B'$$

$$\hookrightarrow m_7 + m_6$$

$$m_{0111} + m_{0011}$$

$$K = f(D_1, D_0, A, B) = m_{12} + m_2 + m_0 + m_9 + m_1 + m_{15} + m_7 + m_{10} + m_2 + m_7 + m_6$$

$$m_7 + m_7 = m_7$$

$$K = \sum m(0, 1, 2, 6, 7, 9, 10, 12, 15)$$

This sum of minterms equations is the same as the other: product of maxterms

$$K = f(D_1, D_0, A, B) = \prod M(3, 4, 5, 8, 11, 13, 14)$$

And the truth table

	D ₁	D ₀	A	B	K
0	0	0	0	0	1
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	0
9	1	0	0	1	1
10	1	0	1	0	1
11	1	0	1	1	0
12	1	1	0	0	1
13	1	1	0	1	0
14	1	1	1	0	0
15	1	1	1	1	1

↳ → Test

⇒ We have solved the
circuit using method I

and method IV
(numerical engine Wolfram Alpha)