 


# Basic sequential building blocks : 1-bit memory cell


## How to infer a D-FF from logic gates?

① The first idea is to use a basic RS-latch





R	S	Q <sup>+</sup> ← next value (future)
0	0	Q current value (present)
0	1	1 Set
1	0	0 Reset
1	1	X (Not defined)

 → This is the structure that has memory to store a bit. R → to reset the output → '0'  
S → to set the output → '1'




RS-latch


Like the standard chip 74LS279

  


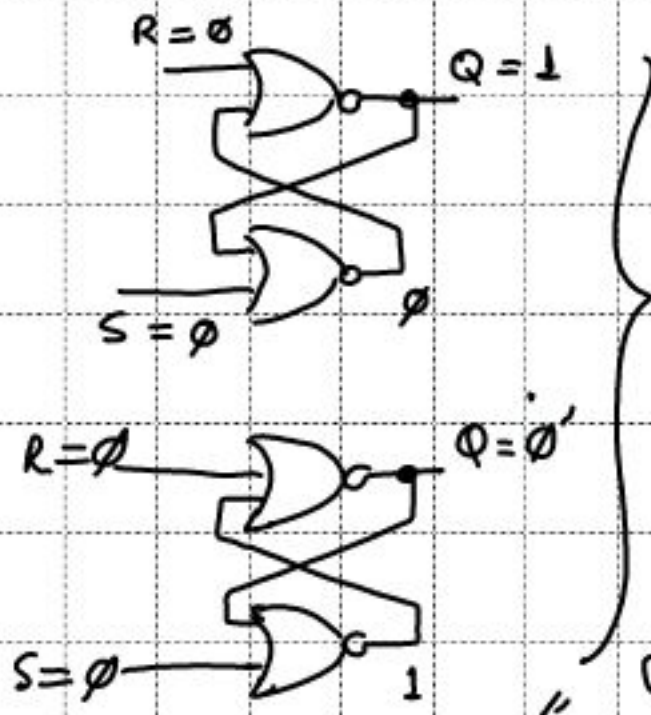
The same function, but with active-low inputs



 
Do nothing  
Q<sup>+</sup> = Q  
Keep the Q value forever  
"memory"




Set Q<sup>+</sup> → '1'  
write a '1'

  

Reset Q<sup>+</sup> → 0  
write a '0'

 

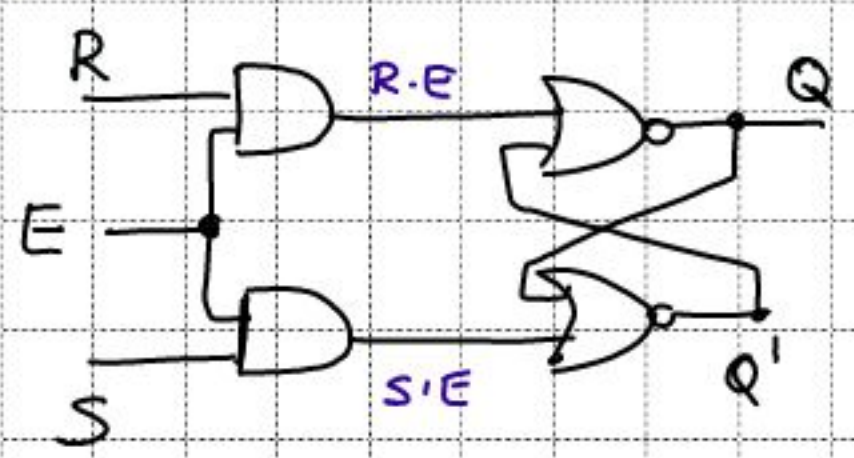
② The RS latch with enable input E (gated latch)



It works in the same way but only when enabled  $E=1$   
 $E=0 \rightarrow$  disabled and the output saved value cannot be changed.


E	R	S	$Q^+$ (next value after propagating input changes)
0	X	X	Q
1	0	0	Q
1	0	1	1 $\rightarrow$ set $Q^+ \rightarrow '1'$
1	1	0	0 $\rightarrow$ reset $Q^+ \rightarrow '0'$
1	1	1	X (Not defined)

 ③ Can we invent an edge (transition detector)



$E = CLK \cdot A = CLK \cdot CLK' \rightarrow '0'$   
 It looks like that the output is always zero

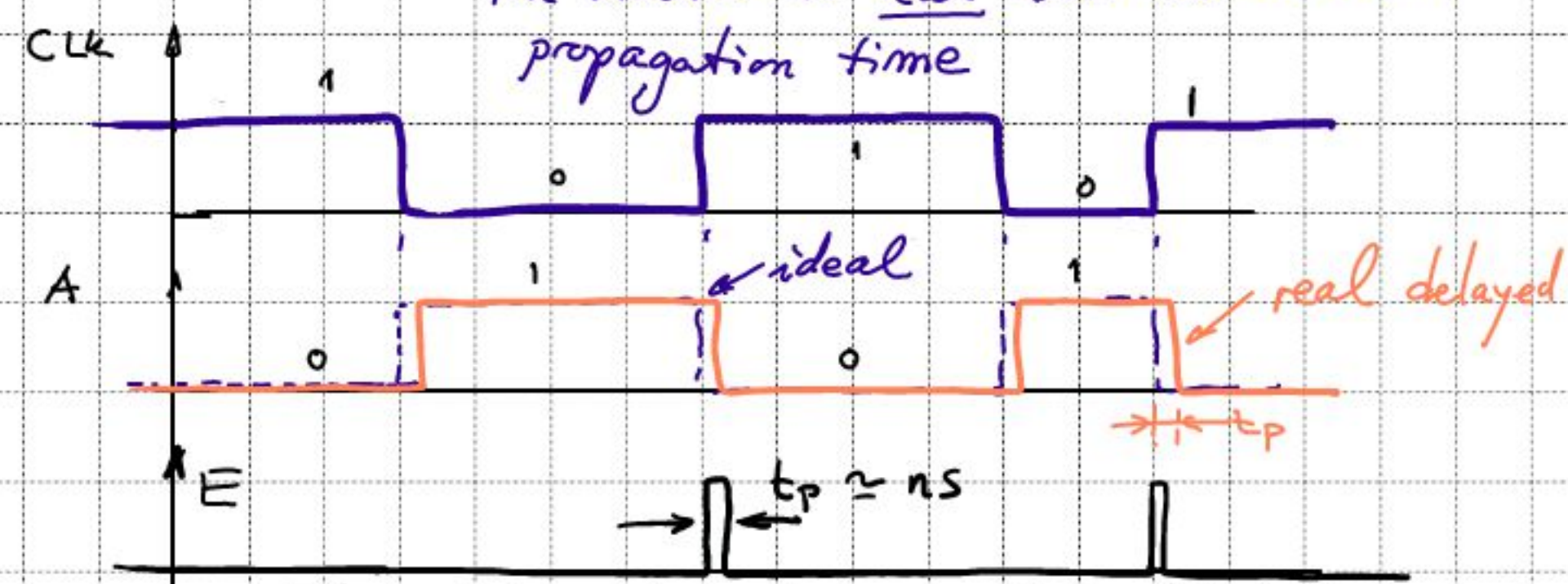The inverter is real  $\rightarrow$  it has a certain propagation time



The rising edge from 0  $\rightarrow$  '1' is detected

④ What if we apply the edge detector circuit to the gated RS latch




There are other ways like the master-slave technique

⇒ The circuit can only save new data when there is a CLK rising edge

→ Note the new inputs CD (Clear direct) and SD (set direct) which don't have to wait for an enable signal to save a '0' or a '1' when active.

 ⇒ } CD → asynchronous reset  
 } SD → asynchronous set



Not known


Do nothing

Thus, we have here a Synchronous RS Flip Flop



RS Flip Flop

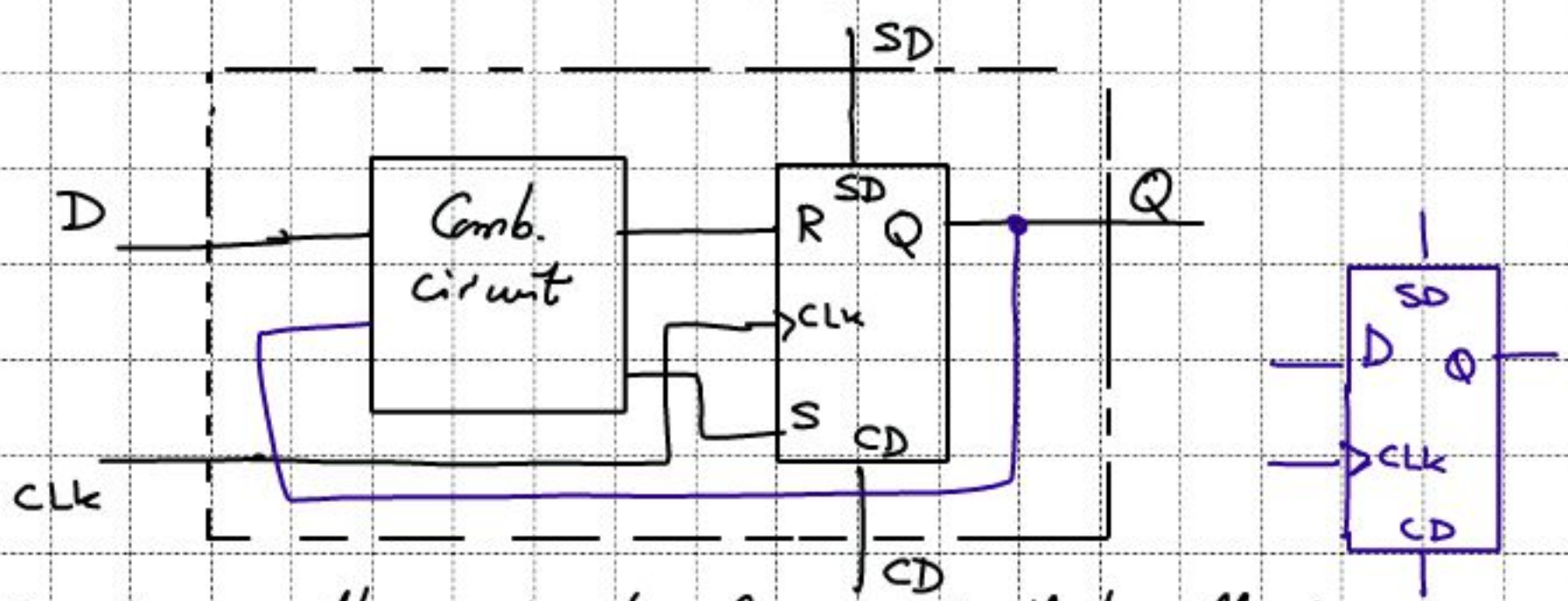⑤ And finally, if we have an RS Flip Flop, how to implement a D-FF (data flip flop)?



Let's deduce the combinational circuit that will drive the RS flip flop inputs.

This is the truth table required:


D	Q	R	S	Q <sup>+</sup>	
0	0	x	0	0	maintain the zero
0	1	1	0	0	Reset
1	0	0	1	1	Set
1	1	0	x	1	maintain the one

This is what we need to apply:

Q	Q <sup>+</sup>	RS
0	0	x0
0	1	01
1	0	10
1	1	0x

This is what we want

 Thus the logic equations:  $R = D'$   
 $S = D$



However, instead of using this demonstrative structural design to build a basic device like the D-FF, we'll use a VHDL behavioural definition which is easily understood by any EDA tool.

⇒ Go back to the web and examine the standard VHDL code for the D-FF that will be used in all the applications