
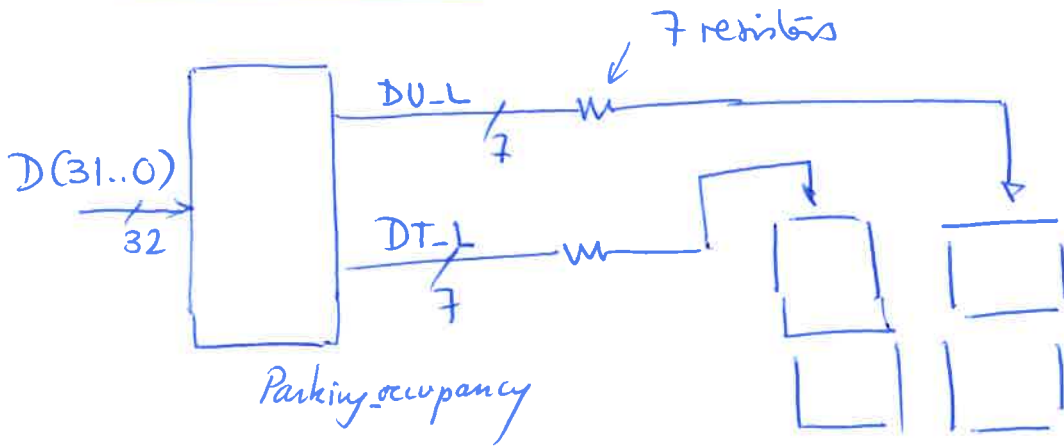


Problem & discussion

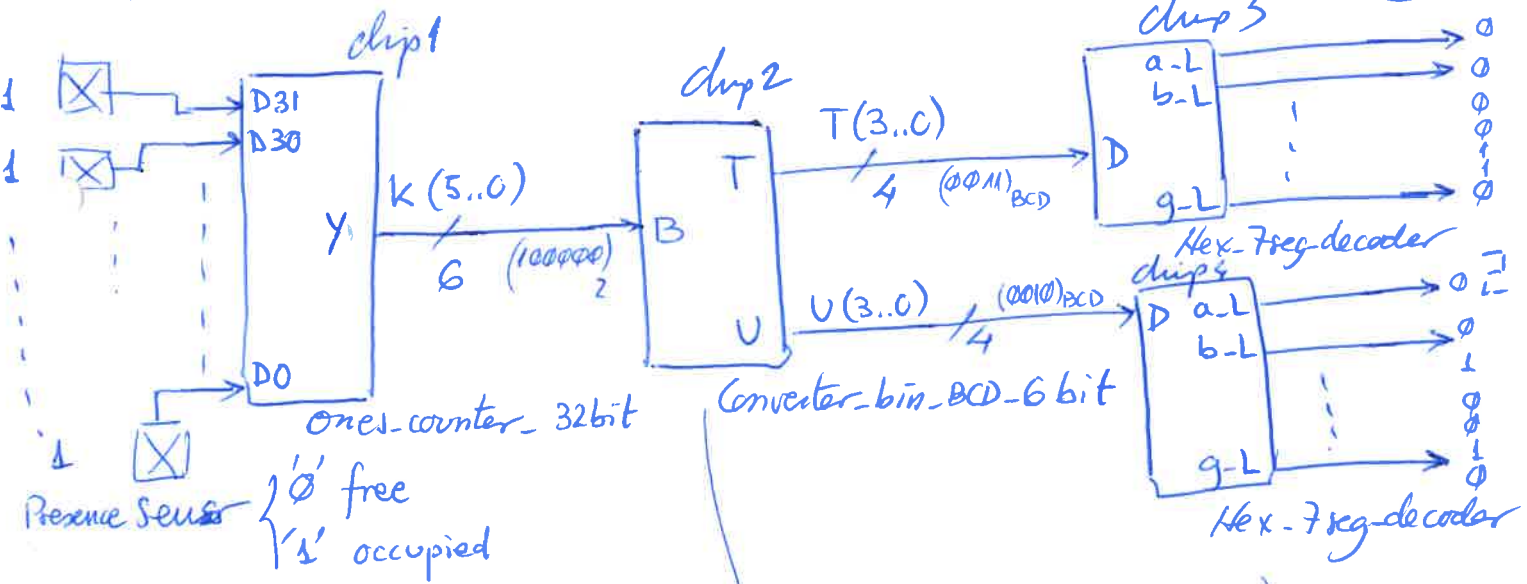

a)



D31	...	D0	K(5..0)
101011...		0101	001100
11		1	100000
00		0	000000

↑ 12 '1's
32 '1's
32 '0's

Tens	Units
B	T U
001100	0001 0010
011111	0011 0001
100000	0011 0010
000111	0000 0111


Translating from binary to BCD

from Hex to 7-seg active low

D	a-L b-L ... g-L
0111	0001111
7	
1001	0001100
5	
0001	0001111

↑ Counting the number of '1' without considering their positions

(b)

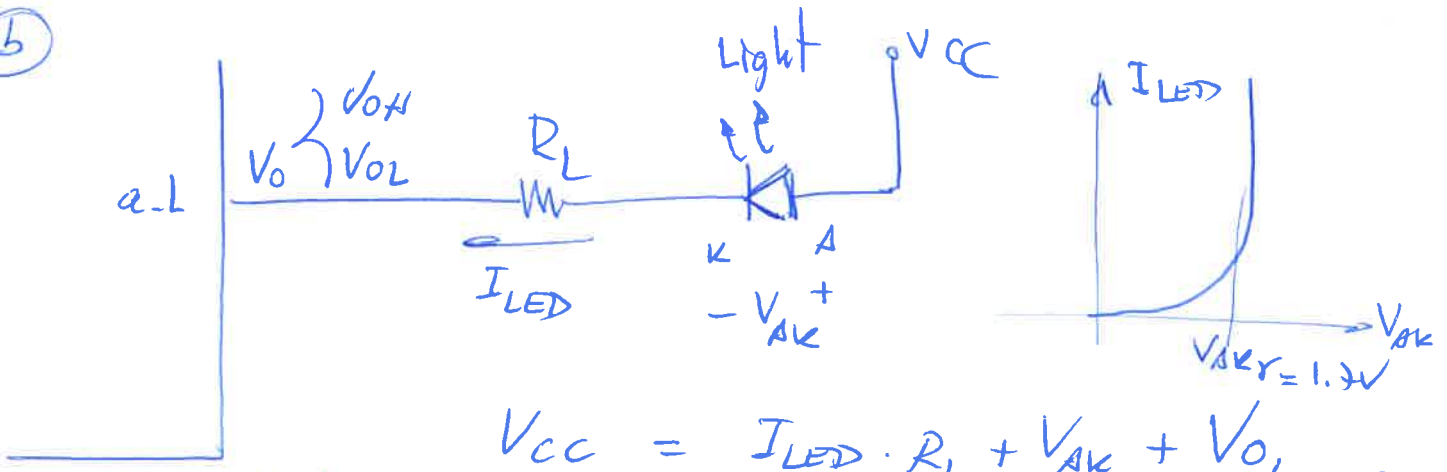


BCD output
Hex-7 segment

$$V_{CC} = I_{LED} \cdot R_L + V_{AK} + V_{OLmax}$$

$$R_L = \frac{V_{CC} - V_{AK} - V_{OLmax}}{I_{LED}}$$

$$R_L = \frac{5V - 1.7V - 0.4V}{15 \mu A} = \underline{193 \Omega}$$


(c)

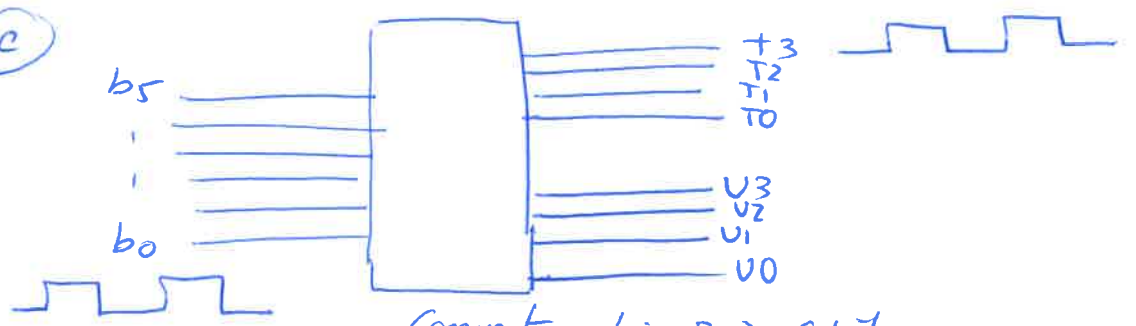


Converter - bin-BCD-6 bit
↑ changing inputs means changing outputs after a delay

POS → equations → 3-levels of gates

$$t_p = 3 \cdot t_{p, \text{gate}}$$

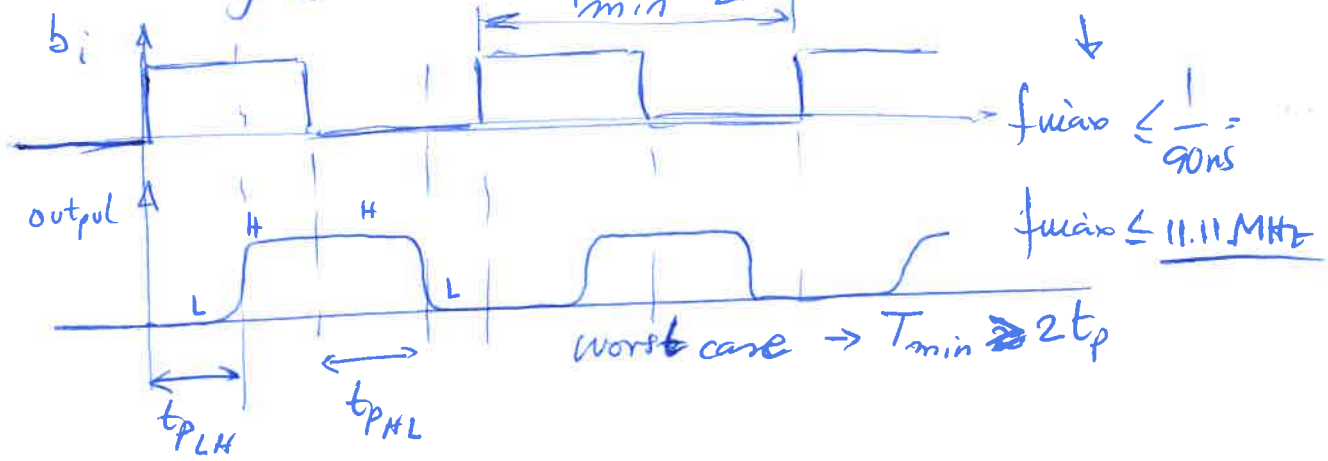


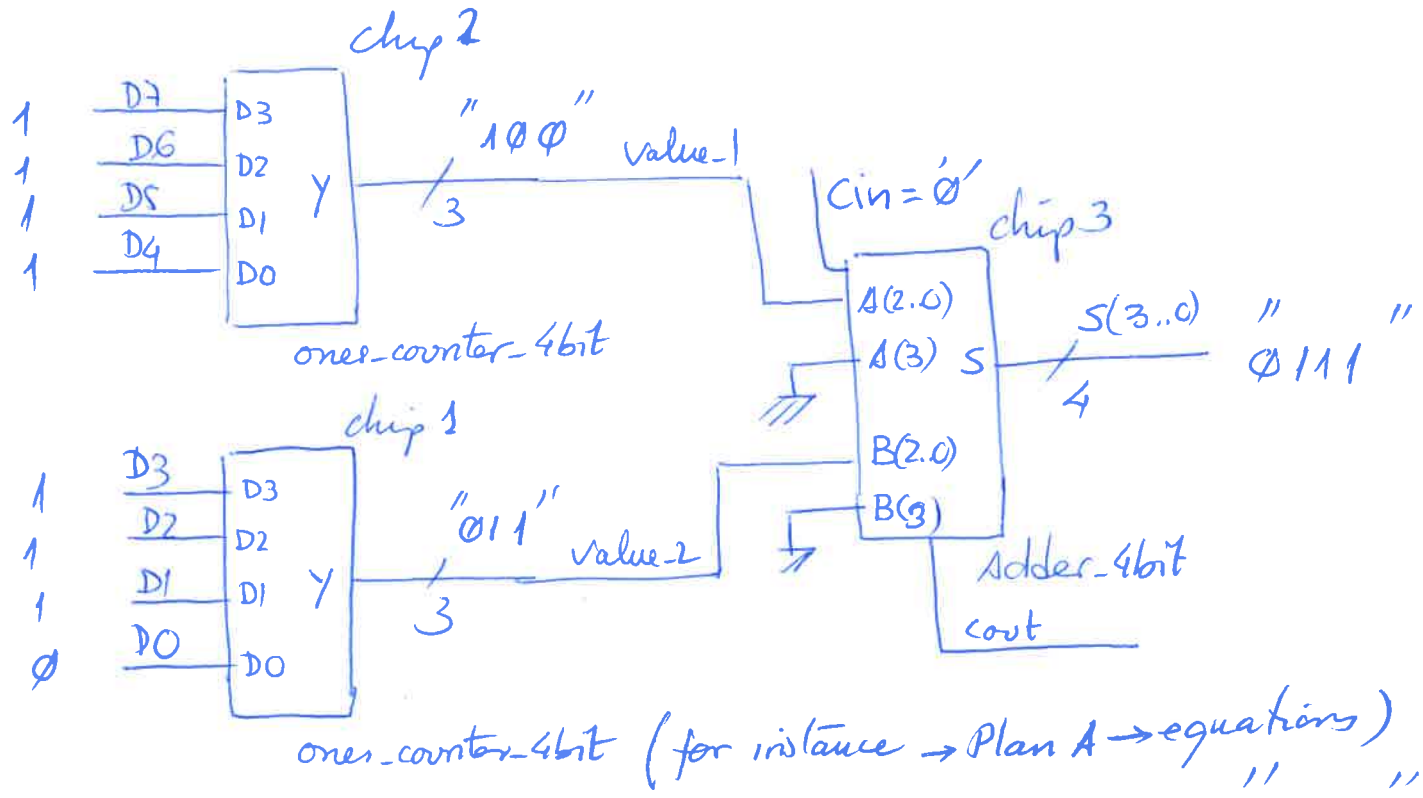d) Let's learn about the way the ones-counter-8bit is build





When counting up to 8 bit 1111 + 1111 -> "1000"
 4 bits are required

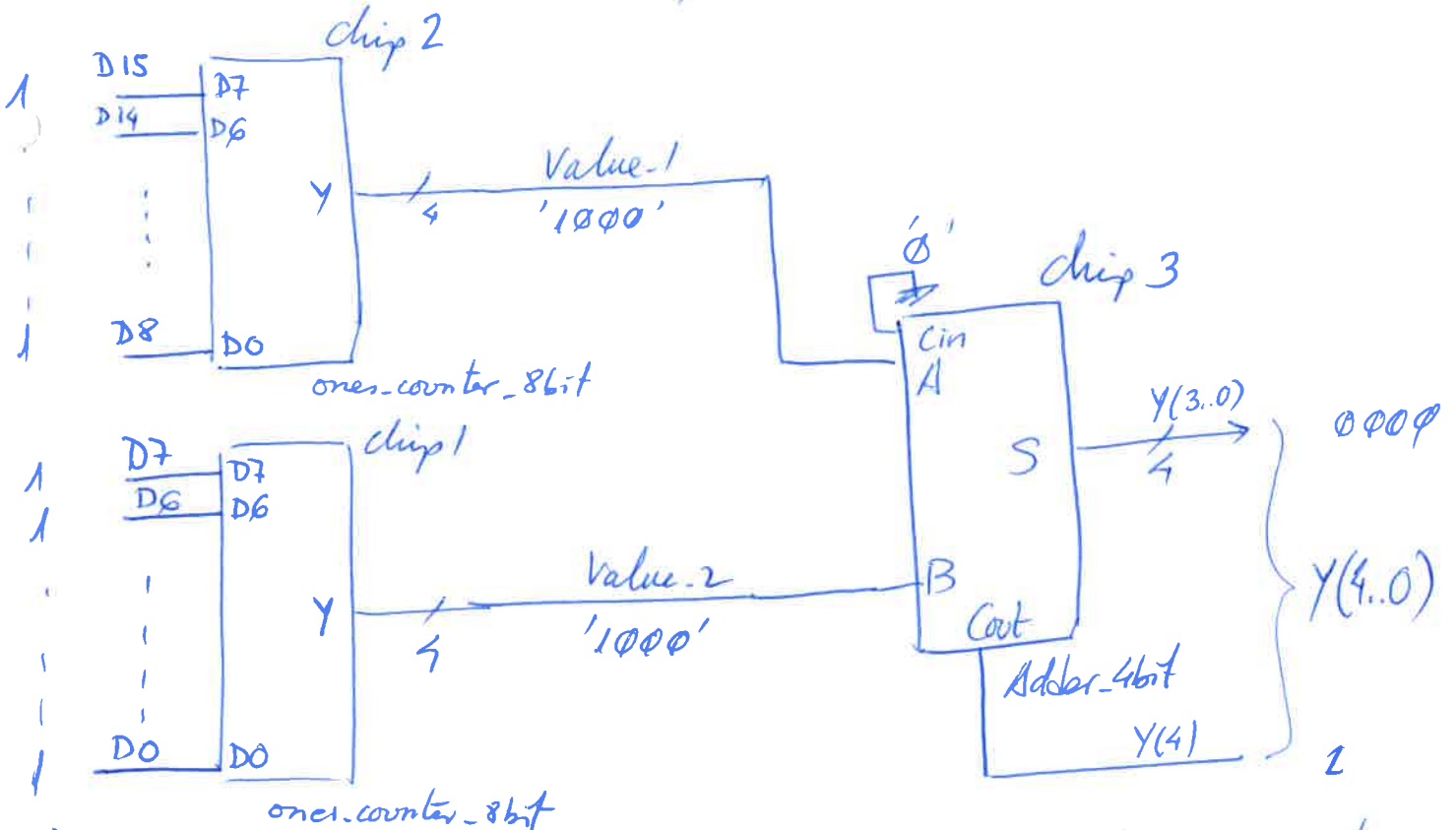Thus, in the same way; we can discuss the ones-counter-16bit:



16 ones means that we need 5 bits "10000"

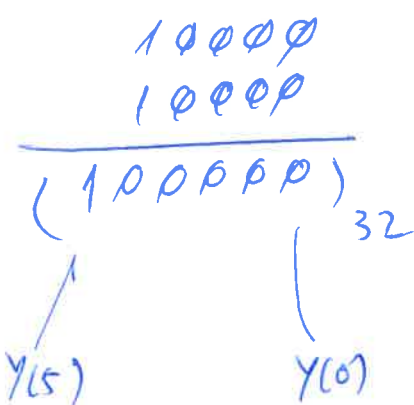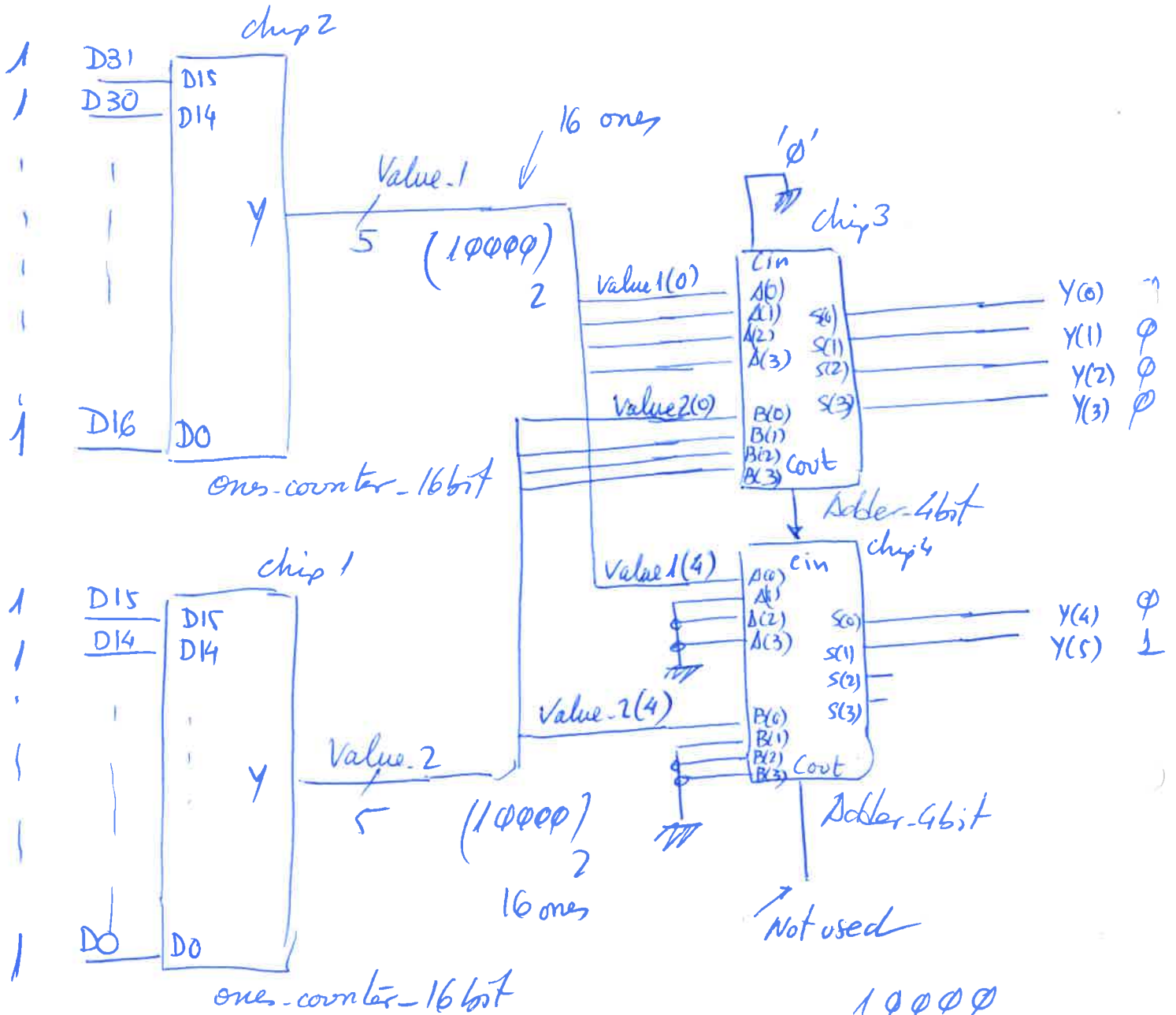So, finally, if the range of the count is 32 bit,
 we need to use an Adder-5bit, for instance using
 two Adder-4bit.



For example 32 ones

The project will include (assuming that the adder-4bit is ripple carry based on Adder-1bit) → 6 VHDL files (adder-1bit, adder-4bit, ones-counter-4bit, ones-counter-8bit, ones-counter-16bit and ones-counter-16bit)