

## Exam solution ideas

### Problem 1

1. Truth table examples of incomplete functions in : [L2.5](#) , [incomplete](#).
2. Only NAND, only NOR circuits are explained in [L1.5](#)
3. MoM is in [L3.3](#) .
4. MoD and decoder expansion examples is in [L3.3](#).
5. Plan B example schematics using capturing the full truth table or the circuit's flowchart are in [LAB2](#).
6. Propagation delay and levels of gates in combinational networks: [L4.3](#).
7. Power consumption is explained in [L4.3](#)
8. How to drive LED is found in [L2.4](#) and basic electrical characteristics in [L1.6](#).

### Problem 2

1. A typical standard binary encoder using plan A is presented in [L2.3](#) and in [Enc 10 4](#)
- 2.
- 3.

### Problem 3

1. A typical 8-bit integer arithmetic circuit for 8bit is discussed in the highlighted project [P4](#).
- 2.
- 3.
- 4.

### Problem 4

The programmable gate is another example of circuit that can be solved using plan C2 and the MoM.

