

Problem 1.

Design a synchronous 5-bit Johnson counter with count enable and reversibility control signals as shown in the symbol in Fig. 1 using the FSM strategy.

 


Fig. 1
Symbol of the sequential system

- Draw the Johnson code for 5 bits. Draw the state diagram indicating both, transitions and outputs
- Draw the FSM structure consisting of CC1 and CC2 and the state register. Indicate its inputs and outputs. How many D_FF will contain the state register if the internal states are coded in binary, and if they are coded in one-hot?
- Draw the CC1 truth table and its equivalent behavioural representation in a flow chart.
- Write the main VHDL sentences of CC2.
- Which is the maximum frequency that can be assigned to the CLK signal when performing a functional simulation?
- Which is the maximum frequency that can be assigned to the CLK signal when performing a gate-level simulation if the target chip is an Altera CPLD Max II EPM2210F324C3 that has the following characteristics:

MAX II Device Features	EPM2210
$t_{PD, gate}$ (ns)	1.7
t_{CO} (ns)	4.6

Problem 2.

Analyse the circuit in Fig. 2 drawing a timing diagram of the outputs **Q(3..0)**. Indicate which may be a possible application of this circuit. How many VHDL files will be required to develop the project?

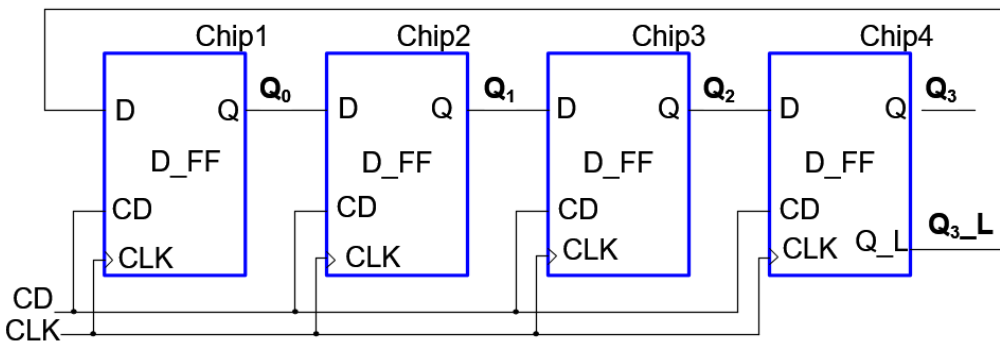


Fig. 2
Circuit based on data flip-flops.

After the rising edge of the CLK

D	Q ⁺
0	0
1	1

Whenever CD = 1
→ Q = 0 immediately

Problem 3.

Fig. 3 shows the symbol of an application based on the PIC18F4520 (Fig. 4) running with an 8 MHz crystal quartz oscillator. The idea is to control the rotation speed of a direct current motor generating a 25 Hz waveform that has 2 possible selectable duty cycles: DC1 = 20% and DC2 = 80%. The 7-segment display will show the sign “-” when idle, and the numbers 1 or 2 depending on the DC selected by the switch. The button **B** starts and stops de waveform generation. Fig. 5 shows an idea of the state diagram.

Fig. 3


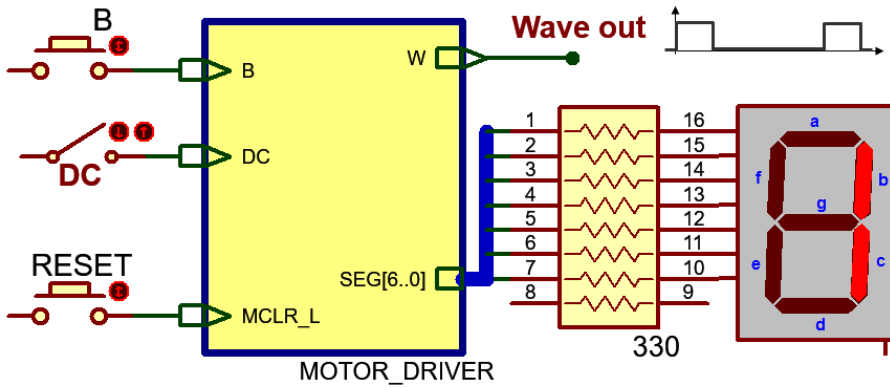


Fig. 4

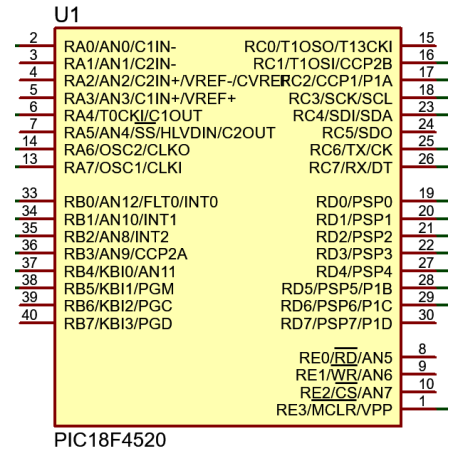

- Draw the two waveforms indicating the T_{ON1} , T_{OFF1} , T_{ON2} and T_{OFF2} periods of time.
- Draw the schematic connecting the inputs and outputs to the PIC18F4520. Add the crystal oscillator and the MCLR_L circuits. Explain how to configure the inputs and outputs in the `init_system()`.
- Explain how to connect and configure the TMR0 (Timer 0) peripheral to generate interrupts. Which are the necessary **N1** and **N2** values for the pre-scaler and the TMR0 counter to be able to generate all the required timing periods?

$$[\text{Timing_period} = (4/F_{osc}) \cdot N1 \cdot N2]$$
- Draw the hardware/software diagram indicating the required RAM variables and how the FSM is solved in software. How to implement the functions `read_inputs()`, `write_outputs()` and `ISR()`? How and where to drive the 7-segment display to show the sign “-” and the numbers “1” and “2” ?
- Complete the state diagram represented in Fig. 5 and deduce the truth tables for the main functions of the C code: `state_logic()` and `output_logic()`.

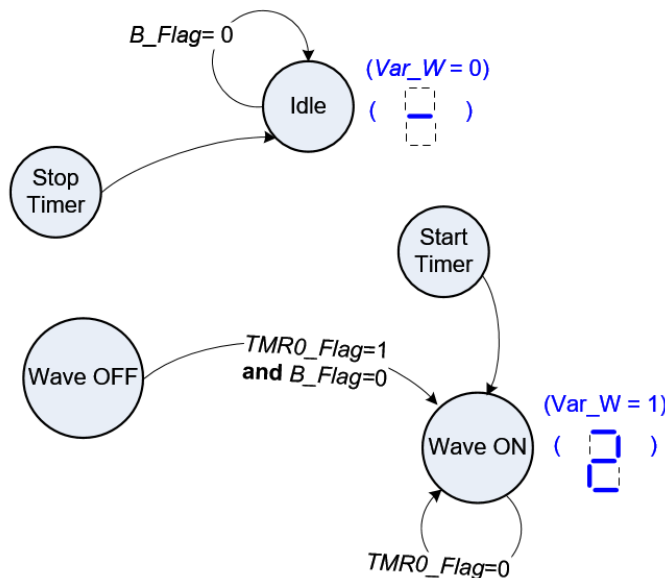


Fig. 5

This is an idea of the state diagram proposed to run this application. It must be completed.

