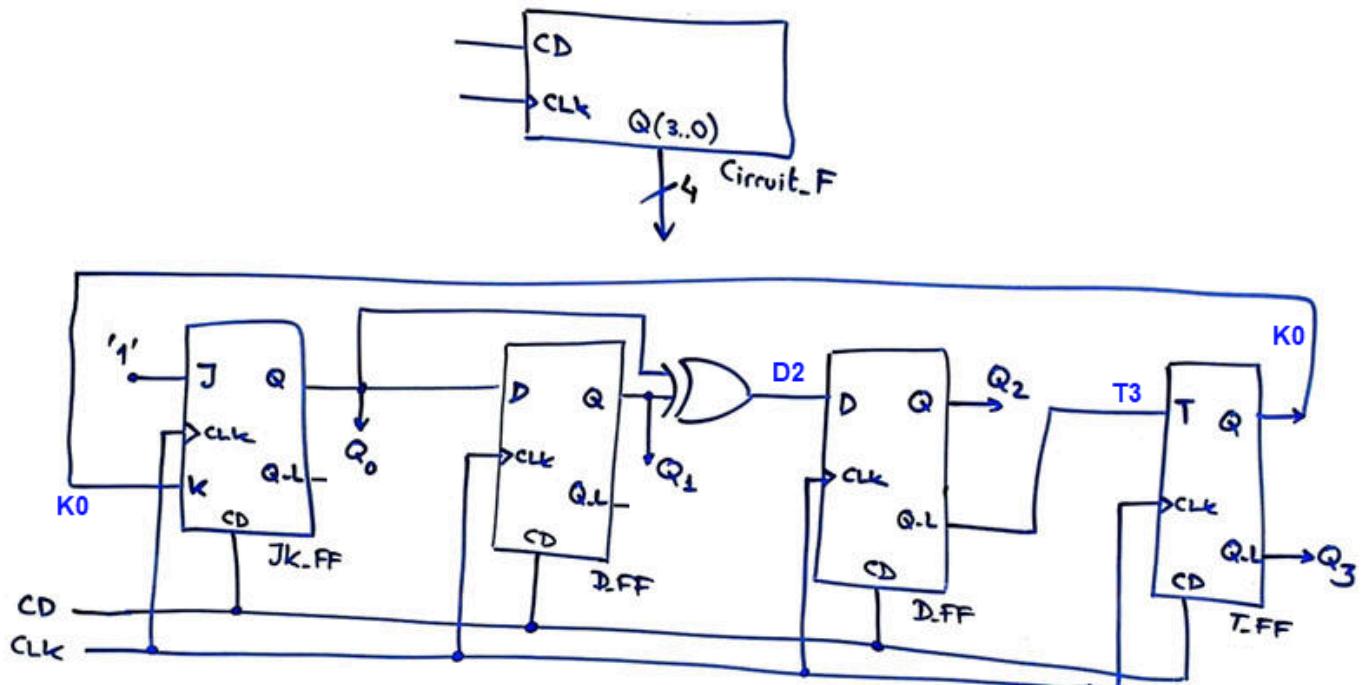


NOTE for all problems and questions: firstly, draw your circuits, sketches and diagrams; secondly, explain your plan and what you do. Justify your results.


Problem 1

(2p)

a) Analyse the circuit in Fig. 1a by means of a timing diagram, this is analysis **method I**, naming all the signals and indicating sampled values on the CLKs' rising edges of interest. Find the binary codes (numbers) generated at the output vector $Q(3..0)$. In this circuit, due to **K0** feedback, you have to consider the evolution of all the flip-flops every **CLK** period.



a)

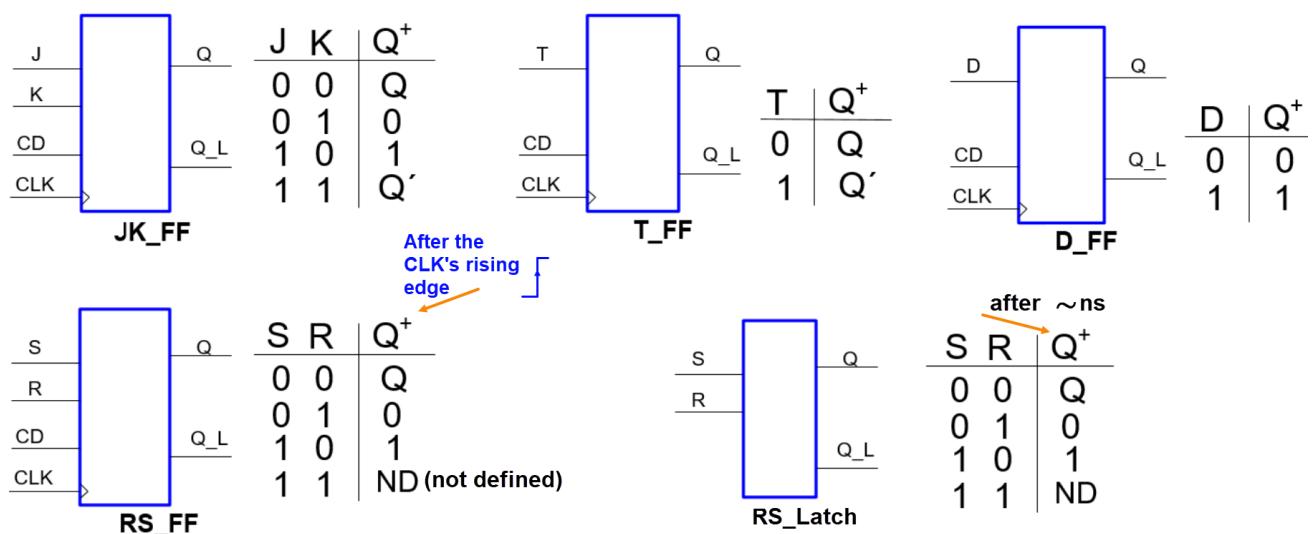

b)

Fig. 1a) *Circuit_F* based on flip-flops. b) *Flip-flop and latch symbols and their functions tables.*

b) Draw the circuit again ready for VHDL translation, as if you liked to obtain the solution performing VHDL ModelSim simulations. How many VHDL files are required in this **plan C2** project?

Problem 2

(4p)

We want to design in VHDL a synchronous 5-bit one-hot code rotator (*rotator_onehot_5bit*) with **CE** and left-right reversibility (**LR_L**) using one of these two strategies: (A) **plan C1** FSM plan or (B) **plan C2** based on counter truncation.

These are the output codes generated when rotating left (**LR_L** = '1'): "00001", "00010", "00100", "01000", "10000", "00001", ...

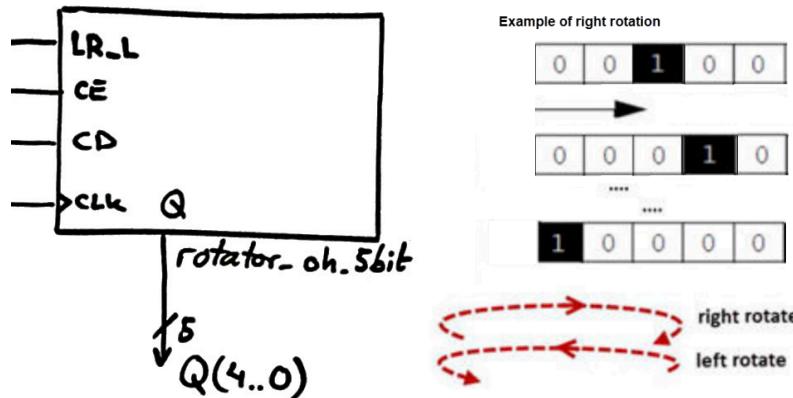


Fig. 2a. Symbol and example of bit rotation when **LR_L** = '0'

a) Draw the circuit's function table. Plot an example of a timing diagram. Draw its **state diagram**.

If you choose the strategy **A**)

- b) Draw the FSM structure consisting of **CC1**, **CC2** and state register, indicating the name of the inputs and outputs. How many **D_FF** are necessary in this application if encoding internal states in one-hot? Draw the internal structure of the state register if the system is encoded in binary radix-2 (sequential).
- c) Write the truth tables for **CC1** and **CC2**. Draw the flowchart for **CC1** and the main ideas on how it is translated into VHDL. How many VHDL files will include this project?

If you choose the strategy **B**)

- b) Plan your circuit using the standard synchronous **Counter_mod16** represented in Fig. 2b and other components.
- c) How many **D_FF** are necessary in this application? How many VHDL files will include this project?

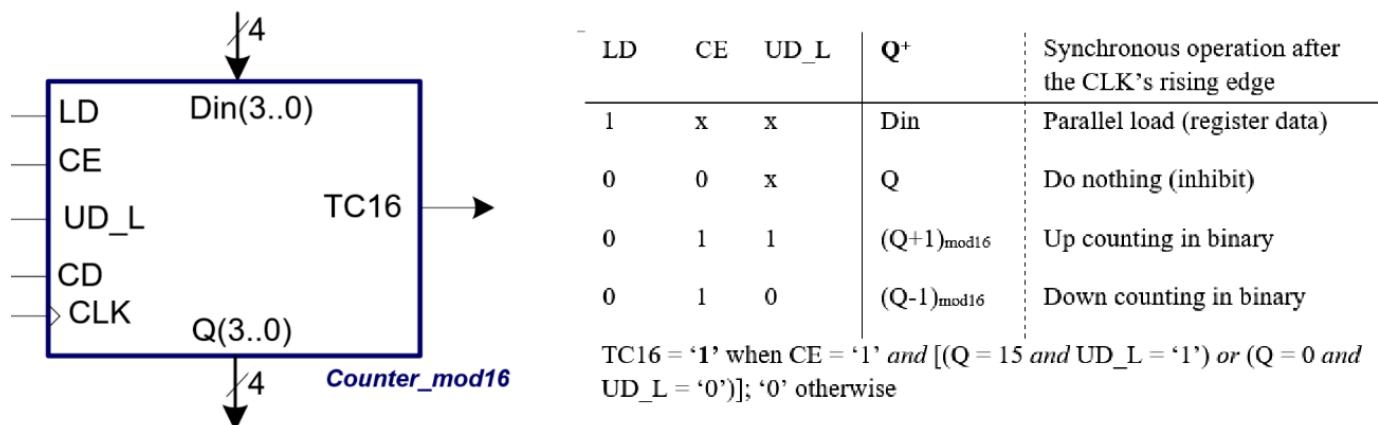


Fig. 2. Symbol and function table of the 4-bit synchronous universal radix-2 counter component that is currently used as a building brick for many applications.

d) Draw a circuit diagram to answer this question: if the **t_{co}** (CLK to output propagation time) of a **D_FF** is 3.4 ns, and the propagation delay **t_p** of a generic logic gate is 2.5 ns, estimate the maximum speed at which your designed rotator can work. Justify your calculations according to your circuit.

Problem 3

(4p)

We will redesign the lamp controller proposed in [LAB6](#) for a microcontroller PIC18F46K22 using our FSM style of programming in C language. For the design phase #1: when clicking the push-button **PB** two times, the lamp **Z** turns ON. When clicking it again another time the lamp turns OFF. Use external interrupts from the push-button **PB**.

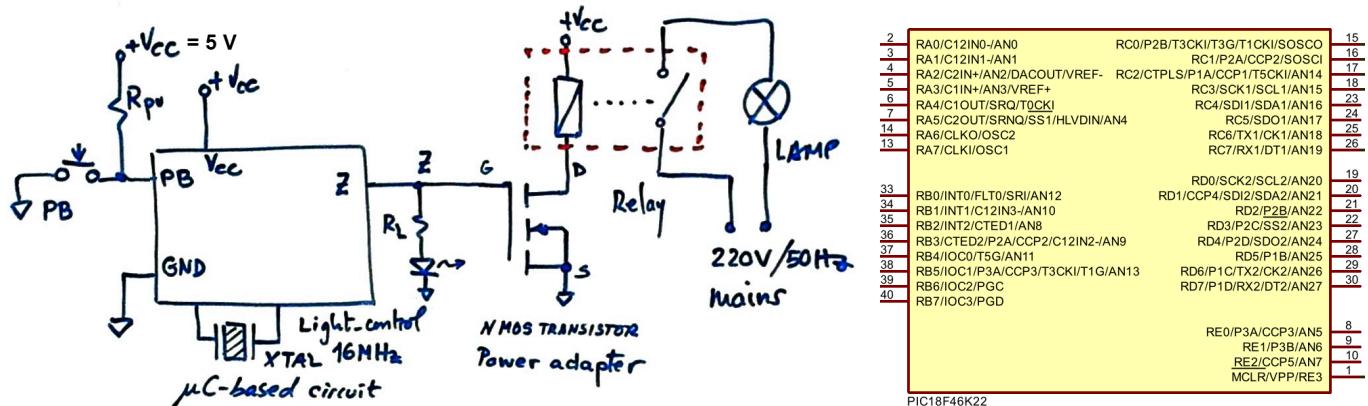


Fig. 3a. Symbol of the lamp controller and the μ C chip from Microchip.

- Draw the electronic schematic to implement the *Light_control* indicating what port pins to use and why. Draw the power-on reset (MCLR_L) circuit and explain how it works. Draw the oscillator circuit using a 16 MHz quartz crystal. Explain the *init_system()* function.
- Draw the list of RAM variables that we will use in this application. Draw the **state diagram**. Organise the main program as a FSM in our CSD way. Explain the interrupt service routine *ISR()*.
- Draw the hardware-software diagram. Solve the function *write_outputs()* using the three column flowchart, memory bitwire operations and C code generated.
- Solve the function *state_logic()* truth table and its flowchart.

For the next design phase #2: The classroom has installed in a ceiling corner a pyroelectric IR presence sensor type Kemet SS-430L-N. It generates a logic '1' when people are detected in the room.

- Explain how the state diagram is modified and draw schematics on how to use the internal TMR0 so that the lamp **Z** will turn OFF automatically to save energy when for 3 minutes people are not detected in the room.

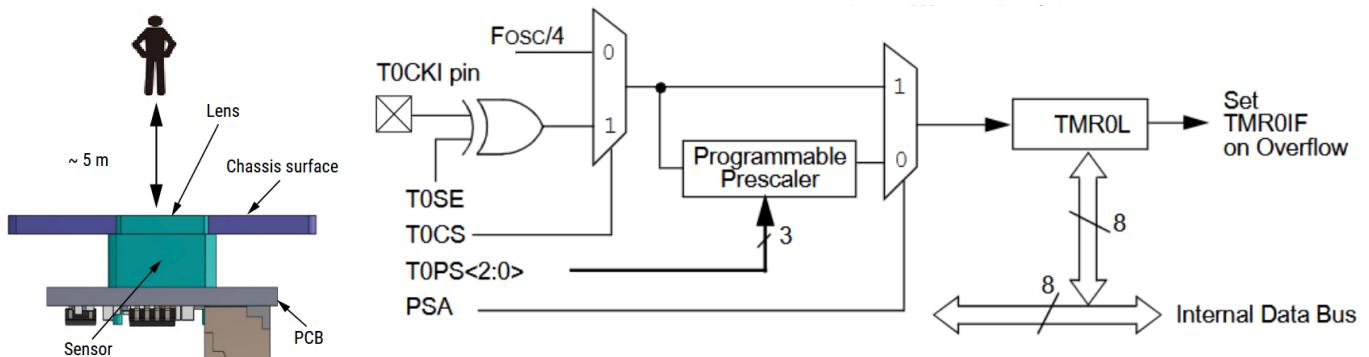


Fig. 3b. The idea of the presence detector and the internal simplified block diagram for the TMR0 peripheral.

► As usual, if you are interested, we invite you to develop, test and prototype these projects in our labs.