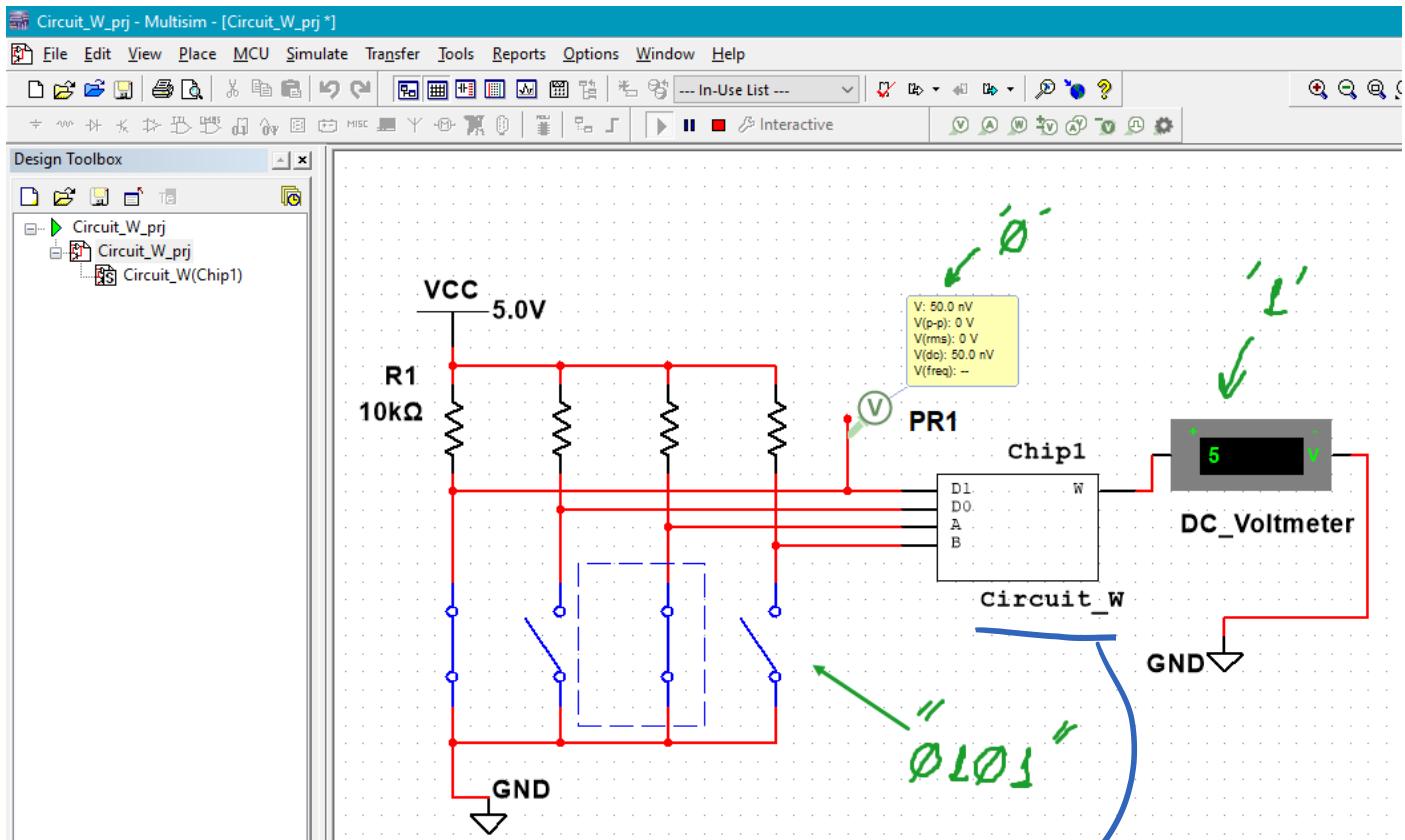
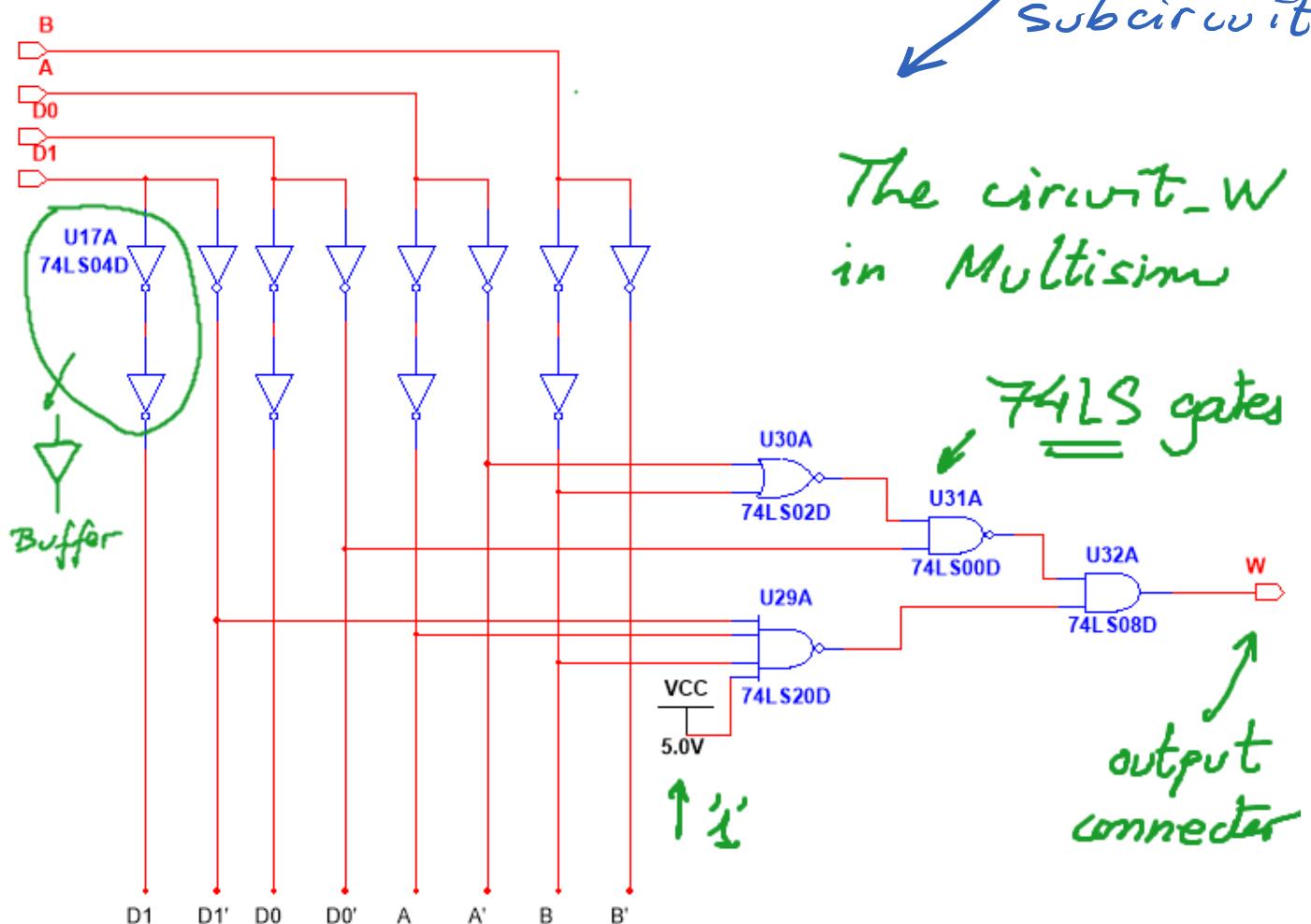


3. Development (method I) → Simulate using MULTISIM the Circuit_W



The circuit_W
in Multisim



You can try all the truth table combinations to obtain $W = f(D_1, D_0, A, B) = \pi M(2, 3, 7, 10)$